

Department of Electrical & Computer Engineering

# Digital Logic And Computing Systems

## Chapter 02 – Logic Gates



Dr. Christophe Bobda

# Agenda

- Basic Gates
- Gate composition
- Possible combinations
- Gates with multiple input
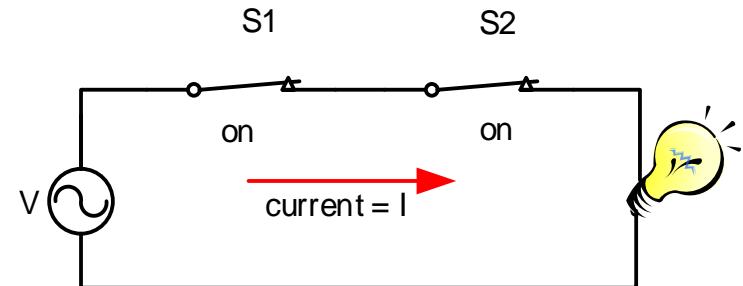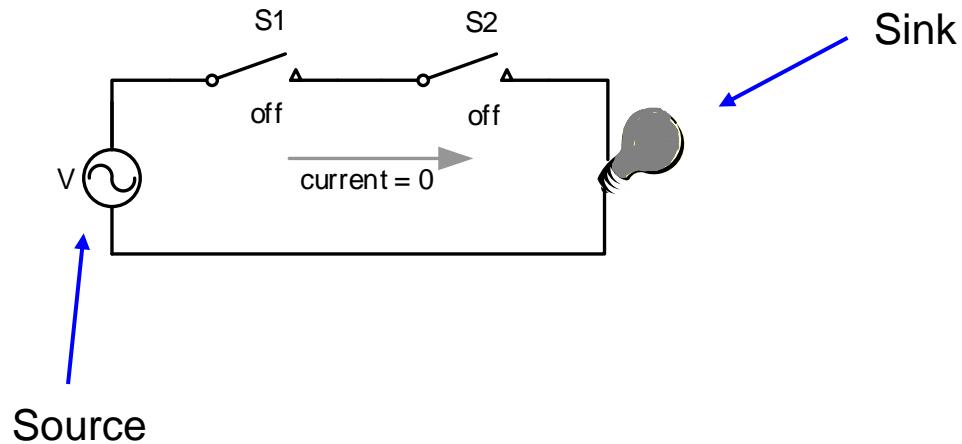
# Basic Gate - Switch


- Switches are basic components used to model digital systems
  - Two possible states: {open, closed} resp. {off, on} resp. {0,1}, {L,H}, {0V,5V}



# Basic Gates – Switch
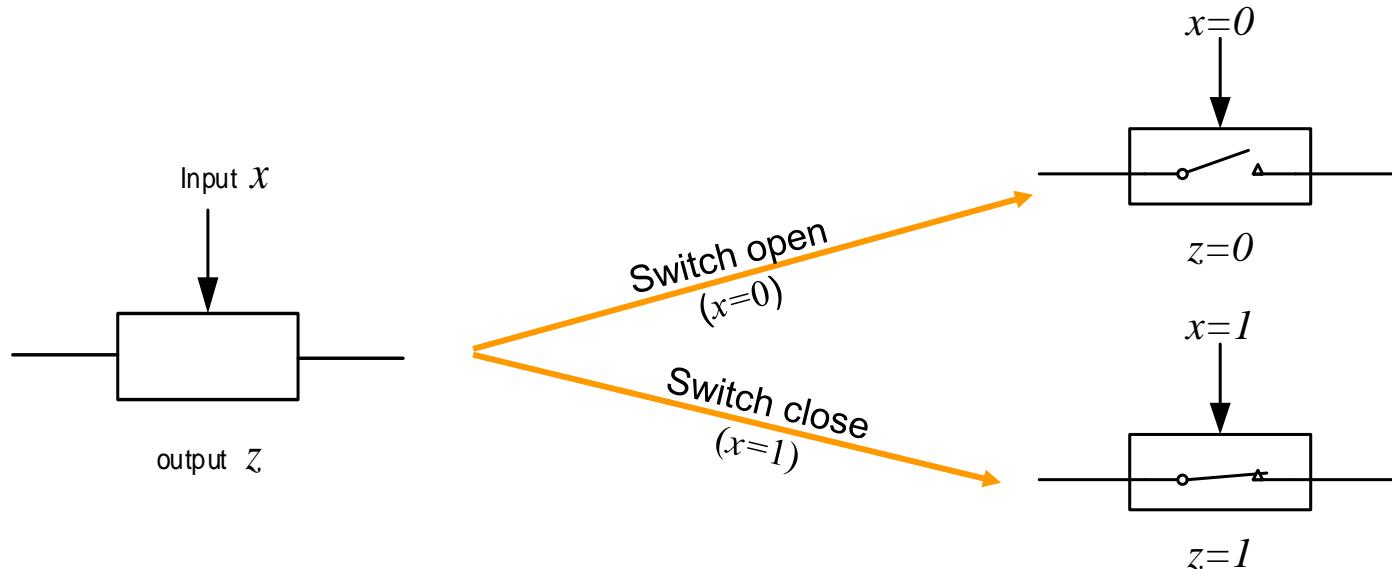
## ■ Modelling ideal switches

- Abstraction:  $x, z$  in  $\{0,1\}$
- Quality (ideal) of switches depends on the technology



# Basic Gates – AND



- “If the weather is nice tomorrow and my brother is available, then we will go swimming”
- We will go swimming ( $z$ ) corresponds to logical conjunction (AND-operation) of
  - $X_1$  = the weather is nice tomorrow and
  - $X_2$  = my brother is available
- AND-Truth table

$x_1$	$x_2$	$z$
0	0	0
0	1	0
1	0	0
1	1	1

- AND-Gates are circuit components that implement AND-operations

# Basic Gates – AND

## ■ Representation: series

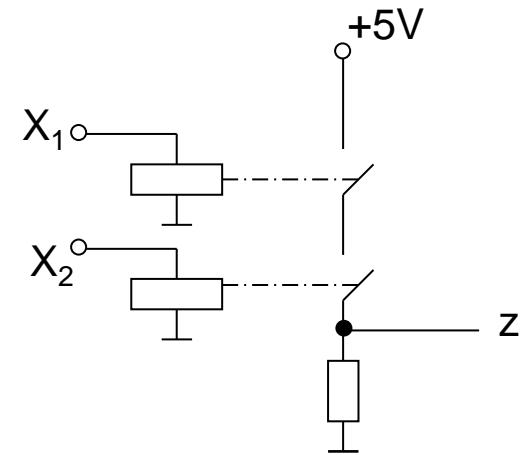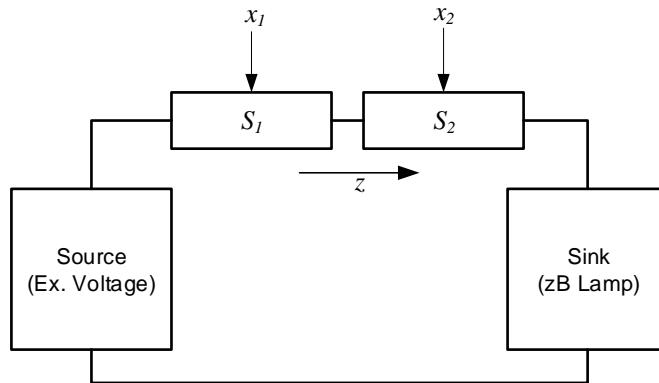

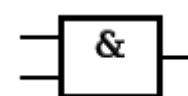
## ■ Notation and Symbol

- Switch (Boolean) algebra:  $Z = X_1 \cdot X_2 = X_1 \wedge X_2 = X_1 \& X_2$



American National Standard Institute (ANSI)



International Electronic Commission (IEC)

# Basic Gates – OR

- “Our party will be successful if many girls attend, or the DJ does a good job”.
- Our party will be successful ( $Z$ ) corresponds to a logical disjunction (OR-operation) of
  - $X_1$  = many girls attend our party and
  - $X_2$  = the DJ does a good job



- Truth table

$x_1$	$x_2$	$z$
0	0	0
0	1	1
1	0	1
1	1	1

- OR-Gates are circuit elements that implement OR-operations



# Basic Gates – OR

## ■ Representation as parallels

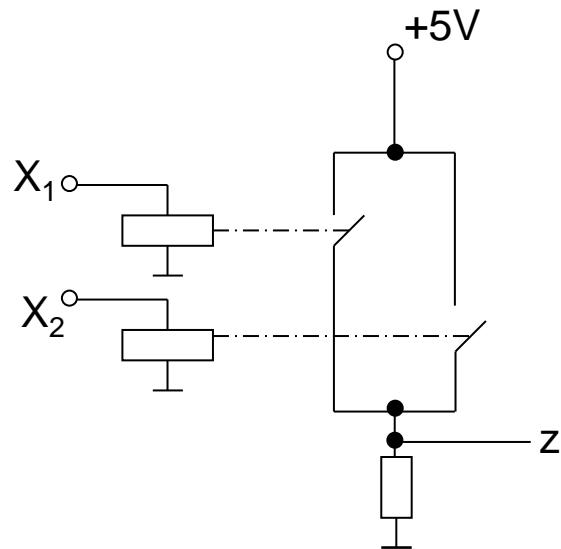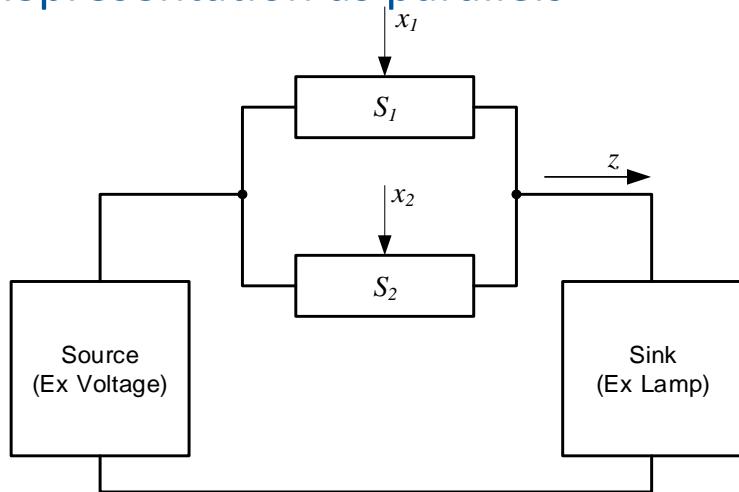
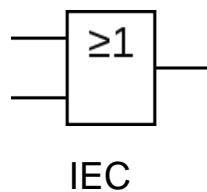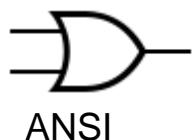
## ■ Notation and Symbol:

- Switch (Boolean) algebra:  $Z = X_1 + X_2 = X_1 \vee X_2$



# Basic Gates – NOT

- “If my mother visits today, then I will not go out”.

- Going out ( $z$ ) is the negation (NOT-relation) of

$X_1$  = My mother visits today



- NOT Truth table

$x_1$	$z$
0	1
1	0

- A NOT-Gate is a circuit that implements the NOT-operation



# Basic Gates – NOT

## ■ Representation

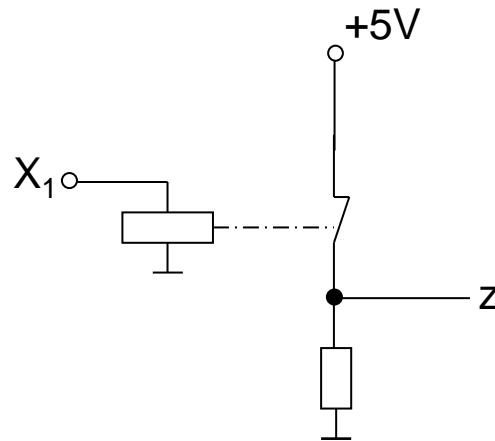 
  
## ■ Notation and Symbol:

- Switch (Boolean)algebra:  $Z = \neg X = \overline{X}$



# Gate Composition – NAND

- A NAND-Gate can be built as serial composition of an AND-Gate and a NOR-gate



- Truth table

$x_1$	$x_2$	$x$	$z$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

- Symbol:

- Switch (Boolean) algebra:  $Z = \overline{X_1 \wedge X_2}$
- The bubble indicates a NOT



ANSI



IEC

# Gate Composition – NOR

- A NOR-Gate can be built as serial composition of an OR-Gate and a NOT-gate



- Truth table


$x_1$	$x_2$	$x$	$z$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

- Symbol:

- Switch (Boolean) algebra:  $Z = \overline{X_1 \vee X_2}$



ANSI

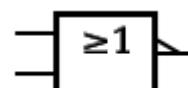


IEC

# Gate Composition – XNOR

- XNOR-Gate (equivalence) has output 1 if and only if the two inputs are equal

- Construction

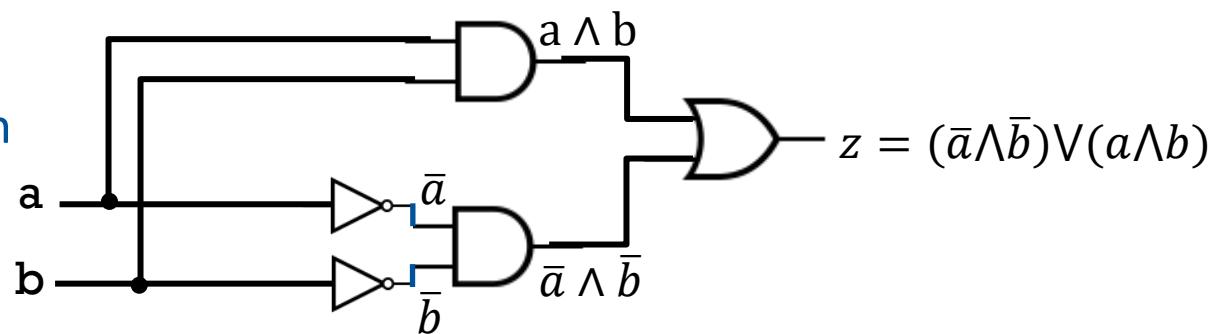


- Truth table

$a$	$b$	$\bar{a}$	$\bar{b}$	$a \wedge b$	$\bar{a} \wedge \bar{b}$	$z$
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

Symbol:




ANSI

 

IEC
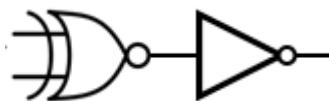
# Gate Composition – XOR

- A XOR-Gate (Exclusive OR) has output 1 if and only if the two inputs are different



- XOR can be built as serial composition of XNOR and NOT gates


- Truth table

$x_1$	$x_2$	$z$
0	0	0
0	1	1
1	0	1
1	1	0

Symbol:



ANSI

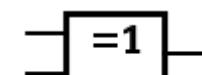



IEC

# Possible Combinations

- 16 possible 2-input functions
  - In general, with n-input:
    - $2^n$  possible result values for 1 functions
    - $2^{2^n}$  possible functions


$x_1$	$x_2$	$z_1$	$z_2$	$z_2$	$z_2$	$z_5$	$z_2$	$z_7$	$z_8$	$z_2$	$z_{10}$	$z_{11}$	$z_{12}$	$z_{13}$	$z_{14}$	$z_{15}$	$z_{16}$
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

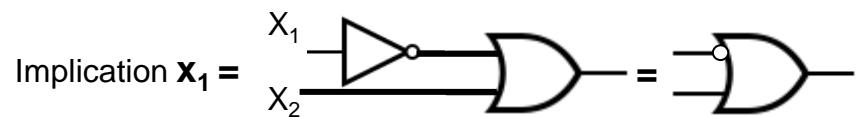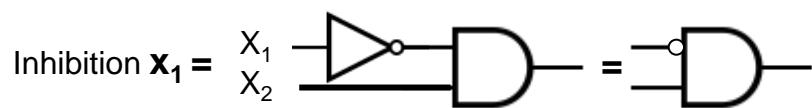Constant 0      NOR      Inhibition  $x_1$       Negation  $x_1$       Inhibition  $x_2$       Negation  $x_2$       XOR      NAND      AND      XNOR      Identity  $x_2$       Implication  $x_1$       Identity  $x_1$       Implication  $x_2$       OR      constant 1


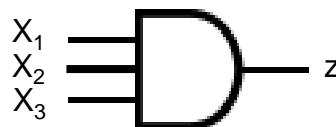
# Gates with more than 2 inputs

- Gates with more than 3 inputs can be implemented as combination of 2-input gates
- for 3 inputs  $x_1, x_2, x_3$ , all 4 cases of  $x_1, x_2$  can be combined with  $x_3 = 0$  and with  $x_3 = 1 \rightarrow 8$  cases ( ie.  $Z = (X_1 \cdot X_2) \cdot X_3$  )
- Example:  $Z = X_1 \wedge X_2 \wedge X_3$



$x_3$	$x_1$	$x_2$	$z$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1



Herbert Wertheim  
College of Engineering  
UNIVERSITY *of* FLORIDA