

Digital Logic and Computer Systems

EEL 3701C

Midterm Exam

Monday, February 24th, 2020

08:20 PM – 10:20 PM

Name: _____

Student ID: _____

Problem 1	Problem 2	Problem 3	Total
/24	/20	/09	/53, %

Problem #1 (General Understanding, 24 pts)

- 1) Why are binary systems preferred to ternary (base-3) despite their optimality? **(1 pts)**

- 2) Name 1 universal gate and explain why it is considered such. Feel free to use Boolean algebra and/or circuit designs in your answer. **(2 pt)**

- 3) In Computing and communication systems, it is often the case that a value stored or transmitted is not the same as the value retrieved or received later.
 - 1) Explain the potential causes? **(1 pts)**

 - 2) Explain an approach to detect cases of fault in such systems **(2 pts)**

- 4) Explain the difference between a flip flop (FF) and a latch **(1 pts)**

5) Why is (S=1, R=1) an invalid input for an SR-FF (**1 pts**)?

6) The following character sequence must be transmitted over a communication line: **DiGiTal**. Using **even** block parity, show the bit sequence that must be transmitted to detect and correct single-bit errors (**6 pts**)?

7) Do the following operation in binary $14.37 - 17.15$ (**4 pts**)

8) Draw the circuit represented by the following VHDL statements (2 pts)

$T1 \leq \text{not } A \text{ and not } B \text{ and } C0;$


$T2 \leq \text{not } A \text{ and } B \text{ and } C1;$

$T3 \leq A \text{ and not } B \text{ and } C2;$

$T4 \leq A \text{ and } B \text{ and } C3;$

$F \leq T1 \text{ or } T2 \text{ or } T3 \text{ or } T4;$

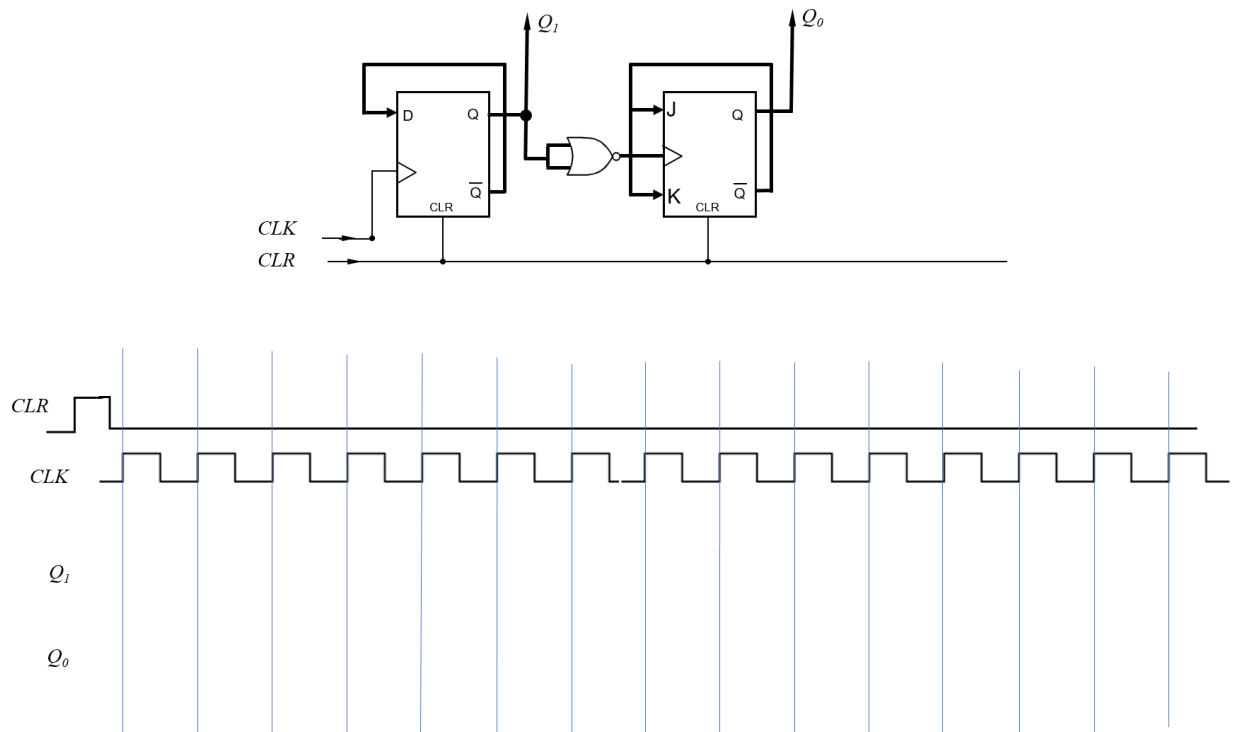9) Given is the following serially connected **D-FF** and **JK-FF**. Complete the timing diagram of the figure below (4 pts)



Problem #2 (Counters, 20 pts)


Using D-FFs for the upper digits of Q_{n-1} - Q_1 , and a JK-FF for Q_0 , draw the circuit diagram of a counter that outputs the following sequence ($6 \rightarrow 8 \rightarrow 9 \rightarrow A \rightarrow C \rightarrow 6$)

Steps to the solution must be clearly visible.

Clearly indicate the outputs of your counter and the interconnections among all basic components used.

Problem #3 (Automata and Control Path, 9 pts)

Use the following diagram for a-d

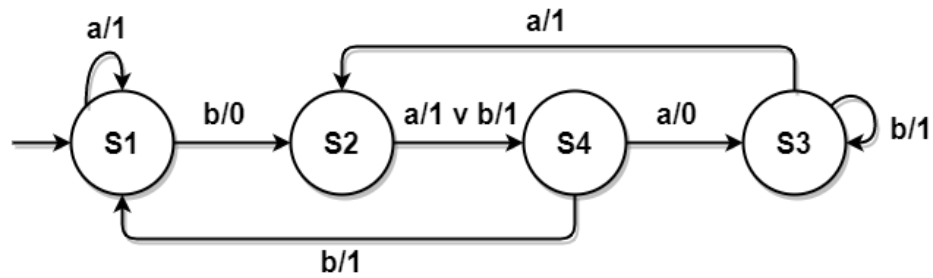

- a) What is the main difference between Moore and Mealy finite state machines? (1 pt)
- b) Draw the state transition table of the automaton in the figure above (2 pts)
- c) If the automaton is a Moore machine, convert it to Mealy. If the automaton is a Mealy machine, convert it to Moore (6 pts)

ASCII

Translation

Table

Dec	Bin	Hex	Char	Dec	Bin	Hex	Char	Dec	Bin	Hex	Char	Dec	Bin	Hex	Char
0	0000 0000	00	[NUL]	32	0010 0000	20	space	64	0100 0000	40	@	96	0110 0000	60	`
1	0000 0001	01	[SOH]	33	0010 0001	21	!	65	0100 0001	41	A	97	0110 0001	61	a
2	0000 0010	02	[STX]	34	0010 0010	22	"	66	0100 0010	42	B	98	0110 0010	62	b
3	0000 0011	03	[ETX]	35	0010 0011	23	#	67	0100 0011	43	C	99	0110 0011	63	c
4	0000 0100	04	[EOT]	36	0010 0100	24	\$	68	0100 0100	44	D	100	0110 0100	64	d
5	0000 0101	05	[ENQ]	37	0010 0101	25	%	69	0100 0101	45	E	101	0110 0101	65	e
6	0000 0110	06	[ACK]	38	0010 0110	26	&	70	0100 0110	46	F	102	0110 0110	66	f
7	0000 0111	07	[BEL]	39	0010 0111	27	'	71	0100 0111	47	G	103	0110 0111	67	g
8	0000 1000	08	[BS]	40	0010 1000	28	(72	0100 1000	48	H	104	0110 1000	68	h
9	0000 1001	09	[TAB]	41	0010 1001	29)	73	0100 1001	49	I	105	0110 1001	69	i
10	0000 1010	0A	[LF]	42	0010 1010	2A	*	74	0100 1010	4A	J	106	0110 1010	6A	j
11	0000 1011	0B	[VT]	43	0010 1011	2B	+	75	0100 1011	4B	K	107	0110 1011	6B	k
12	0000 1100	0C	[FF]	44	0010 1100	2C	,	76	0100 1100	4C	L	108	0110 1100	6C	l
13	0000 1101	0D	[CR]	45	0010 1101	2D	-	77	0100 1101	4D	M	109	0110 1101	6D	m
14	0000 1110	0E	[SO]	46	0010 1110	2E	.	78	0100 1110	4E	N	110	0110 1110	6E	n
15	0000 1111	0F	[SI]	47	0010 1111	2F	/	79	0100 1111	4F	O	111	0110 1111	6F	o
16	0001 0000	10	[DLE]	48	0011 0000	30	0	80	0101 0000	50	P	112	0111 0000	70	p
17	0001 0001	11	[DC1]	49	0011 0001	31	1	81	0101 0001	51	Q	113	0111 0001	71	q
18	0001 0010	12	[DC2]	50	0011 0010	32	2	82	0101 0010	52	R	114	0111 0010	72	r
19	0001 0011	13	[DC3]	51	0011 0011	33	3	83	0101 0011	53	S	115	0111 0011	73	s
20	0001 0100	14	[DC4]	52	0011 0100	34	4	84	0101 0100	54	T	116	0111 0100	74	t
21	0001 0101	15	[NAK]	53	0011 0101	35	5	85	0101 0101	55	U	117	0111 0101	75	u
22	0001 0110	16	[SYN]	54	0011 0110	36	6	86	0101 0110	56	V	118	0111 0110	76	v
23	0001 0111	17	[ETB]	55	0011 0111	37	7	87	0101 0111	57	W	119	0111 0111	77	w
24	0001 1000	18	[CAN]	56	0011 1000	38	8	88	0101 1000	58	X	120	0111 1000	78	x
25	0001 1001	19	[EM]	57	0011 1001	39	9	89	0101 1001	59	Y	121	0111 1001	79	y
26	0001 1010	1A	[SUB]	58	0011 1010	3A	:	90	0101 1010	5A	Z	122	0111 1010	7A	z
27	0001 1011	1B	[ESC]	59	0011 1011	3B	;	91	0101 1011	5B	[123	0111 1011	7B	{
28	0001 1100	1C	[FS]	60	0011 1100	3C	<	92	0101 1100	5C	\	124	0111 1100	7C	
29	0001 1101	1D	[GS]	61	0011 1101	3D	=	93	0101 1101	5D]	125	0111 1101	7D	}
30	0001 1110	1E	[RS]	62	0011 1110	3E	>	94	0101 1110	5E	^	126	0111 1110	7E	~
31	0001 1111	1F	[US]	63	0011 1111	3F	?	95	0101 1111	5F	_	127	0111 1111	7F	[DEL]