

Digital Logic and Computer Systems
EEL 3701C **Midterm Exam** **Friday, October 30, 2020**
08:20 PM – 10:20 PM

Name: _____

Student ID: _____

Location: Zoom

<https://ufl.zoom.us/j/92232023106?pwd=M0hhZERuWVFsanFYeXg0dmVOcDZFUT09>

Rules for the exam

1. **Be in zoom** the entire time with your camera on but mic muted. If possible, please be alone in a quiet room with no distractions.
2. You will be placed in a breakout room with a randomly selected PI. If you have a question, please send a direct message to the PI in your room.
3. **Open note and open internet** (including canvas!)
4. However, communication with others is **strictly prohibited**. This includes but is not limited to text, IM (such as Discord, Snapchat, Facebook, etc.), email, voice chat, etc. Violations of this will be treated as a violation of the UF Academic Policy.
5. You **may complete the exam in any way** that best suits you. You can print out the exam and write on it, you can use notebook paper, you can use a tablet+stylus on your computer, whatever works. Please **clearly mark each problem** in your submission.
6. You are allotted an **extra 15 minutes** on the due date for printing, scanning, and any technical issues. However, **do not use this as extra time**. You are expected to stop working at 10:20pm.
7. **Show all work!!**
8. When scanning, please make sure that **all answers are legible** and clear in the photos. This does not have to apply for work you do, but we do give **partial credit** for correct work so keep that in mind.
9. Please keep all truth tables in **counting order**


On my honor, I have neither given nor received unauthorized aid in doing this assignment.

Signature: _____

Problem 1	Problem 2	Problem 3	Total
/31	/15	/15	/61, %

Problem #1 (General Understanding, 35 pts)

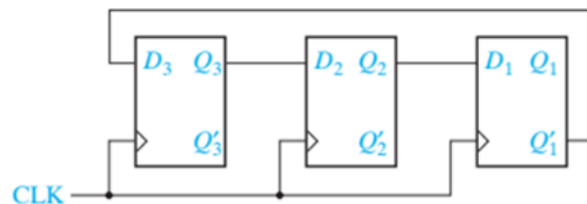- 1) What is the difference between combinational and sequential circuits? **(1 pts)**
- 2) Why are binary numbers used in digital systems, as opposed to other bases? **(1 pts)**
- 3) In digital systems, why are 1's Complement and 2's Complement commonly used to represent negative numbers instead of signed magnitude? **(1 pts)**
- 4) The following figure shows a 3-bit end-around shift register with the Q_1' output from the last flip-flop fed back into the D input of the first flip-flop. For example, if the initial state of the flip flop is 000, then the next state will be 100.




Provide the next three successive states ($D_3D_2D_1$) of the shift register assuming a starting point of 100. **(3 pt)**

- 5) We wish to develop an analog controller for a safety relief valves for thermal, hydraulic, and domestic water systems. We will use the CalfiT 311 series that outputs the following values in bar: {1.5, 2, 2.5, 3, 3.5, 4, 5, 5.5, 6, 7, 8, 9} bar. Note that bar is a unit for pressure.

Create a viable binary encoding of the output values by creating a table with the bar value in one column and its encoded binary representation in the other. Then, explain why you chose this encoding in 1-2 sentences. **(5 pt)**

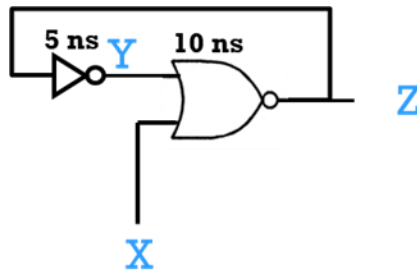- 6) Draw a timing diagram for the circuit following circuit, showing X, Y, and Z. Assume that X is initially 0, and Y is initially 1., after After 10 ns X becomes 1 for 80 ns, and then X is 0 again. Use the gate propagation delays shown in the diagram. **(6 pts)?**



- 7) Do the following operation in binary **23.15 + 31.11**.
Limit your fractional decimal conversion to 4 digits after the decimal point. **(6 pts)**

- 8) Do the following conversions
- a) 478_9 to XXX_{11} **(5 pts)**


- b) 56789_{16} to X_{64} (Note: A base-64 table is provided on the last page of this exam) **(3 pts)**

Problem #2 (Counters, 15 pts)

Create a 3-bit counter using a JK-FF for the least significant bit, an SR-FF for the middle bit, and a D-FF for the most significant bit. The counter should follow the sequence $1 \rightarrow 3 \rightarrow 2 \rightarrow 6 \rightarrow 7 \rightarrow 5 \rightarrow 1$. For any values **not defined** in the sequence, the next value does not matter.

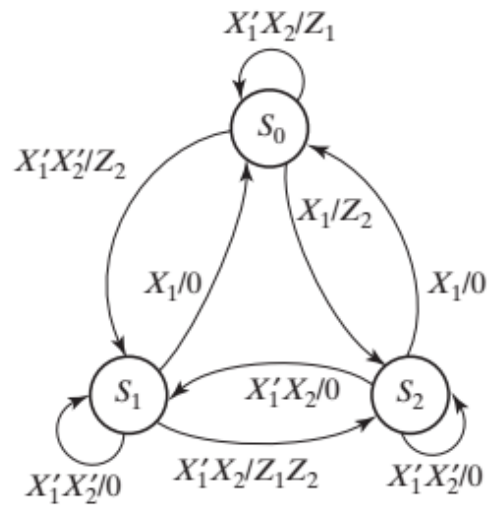Problem #3 (Automata and Control Path, 15 pts)

Given an automaton represented through the following state transition diagram



a) Devise the state transition table of the automaton **(5 pt)**

b) Convert the automaton into its Moore equivalent **(10 pts)**

Base-64 Conversion Table

For 10b

Dec	Hex	Base-64	Dec	Hex	Base-64
0	00	0	32	20	W
1	01	1	33	21	X
2	02	2	34	22	Y
3	03	3	35	23	Z
4	04	4	36	24	a
5	05	5	37	25	b
6	06	6	38	26	c
7	07	7	39	27	d
8	08	8	40	28	e
9	09	9	41	29	f
10	0A	A	42	2A	g
11	0B	B	43	2B	h
12	0C	C	44	2C	i
13	0D	D	45	2D	j
14	0E	E	46	2E	k
15	0F	F	47	2F	l
16	10	G	48	30	m
17	11	H	49	31	n
18	12	I	50	32	o
19	13	J	51	33	p
20	14	K	52	34	q
21	15	L	53	35	r
22	16	M	54	36	s
23	17	N	55	37	t
24	18	O	56	38	u
25	19	P	57	39	v
26	1A	Q	58	3A	w
27	1B	R	59	3B	x
28	1C	S	60	3C	y
29	1D	T	61	3D	z
30	1E	U	62	3E	#
31	1F	V	63	3F	%

Table 1 – Base-64 conversion table. Note: Base-64 is case sensitive!