

Department of Electrical & Computer Engineering

# Digital Logic And Computing Systems


## Chapter 03 – Combinational Circuit Design

Dr. Christophe Bobda

# Agenda

- ❑ Combinational Circuits
- ❑ Synthesis of Combinational Circuits
- ❑ Logic-Optimization
  - Simplification Theorem
  - Canonical- and Normal Forms
  - Karnaugh-Method
  - Quine-McCluskey Algorithm

# Combinational Circuits

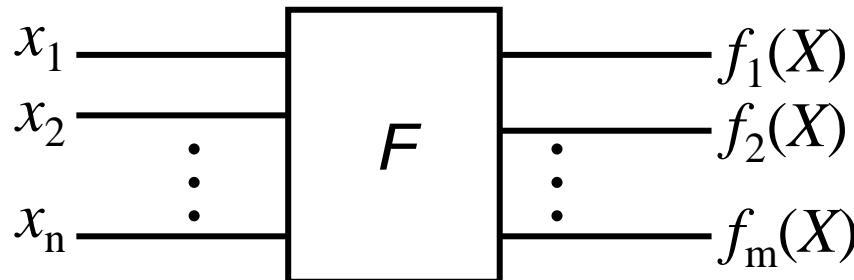



- ❑ Definition: A logic circuit with  $n$  inputs  $X = (x_1, x_2, \dots, x_n)$  and  $m$  outputs,  $m \geq 1$ , whereas  $F(X) = (f_1(X), f_2(X), \dots, f_m(X))$ , is called **combinational circuit**, if and if  $F(X)$  is solely defined at a given time by the inputs  $X$  value at that time.
  - Every change in the inputs instantaneously impacts the outputs.
  - A combinational circuit has **no memory**.
    - Previous input values cannot be recalled.

# Delays

- ❑ Gates and signals have delays. Information is saved for a very short period of time

- ❑ Timing diagram: ideal gate

- ❑ In reality

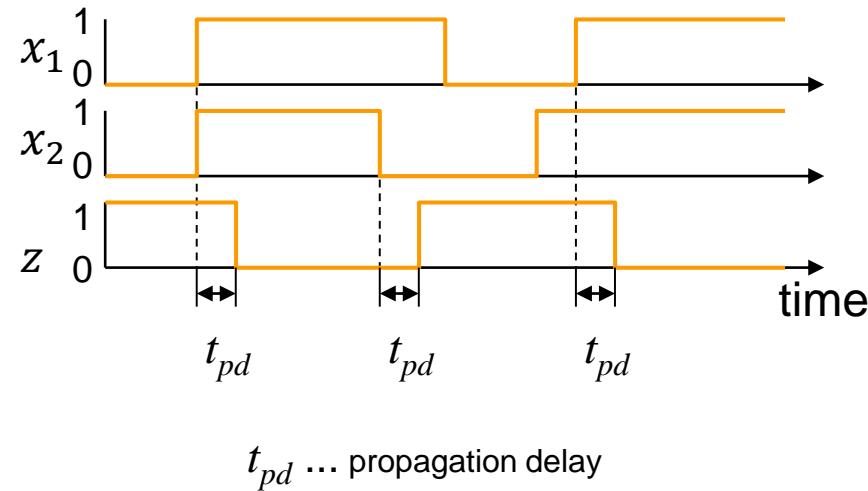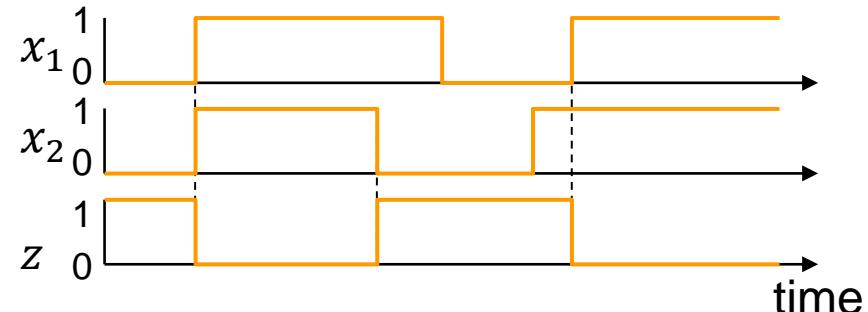

# Synthesis of Digital Circuits

- ❑ Design and implementation of circuits to perform a given function
  - Given: Specification; Library: AND, NOR, NOT, etc....
  - Result: A circuit that implements the specification with the library elements
- ❑ Synthesis steps
  1. Define the inputs and outputs of the circuit
  2. Draw a truth table for every output as a function of all inputs
    - a) Compute the logic expression for every output
    - b) Minimize the expression if needed
  3. Use available library elements to assemble your circuit
    - Possible transformation needed

# Synthesis of Digital Circuits

- ❑ Example: Circuit to control an elevator
  - Goal: Prevent riding under dangerous conditions (door open)
    - Ride only possible if the door is closed and the load is under limit
- ❑ Step 1: Define Inputs and Outputs
  - A → Door ( $A = 0 \rightarrow$  door open,  $A = 1 \rightarrow$  door closed)
  - B → Weight ( $B = 1 \rightarrow$  above limit,  $B = 0 \rightarrow$  below limit)
  - C → Button ( $C = 1 \rightarrow$  button pressed,  $B = 0 \rightarrow$  button not pressed)
  - Z → Output ( $Z = 1 \rightarrow$  engine on,  $Z = 0 \rightarrow$  engine off)

# Synthesis of Digital Circuits

## ❑ Step 2:


- Truth table

A	B	C	z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

- Logic expression

$$Z = A \wedge \overline{B} \wedge C$$

- No more reduction needed

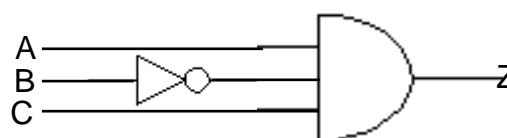


# Synthesis of Digital Circuits
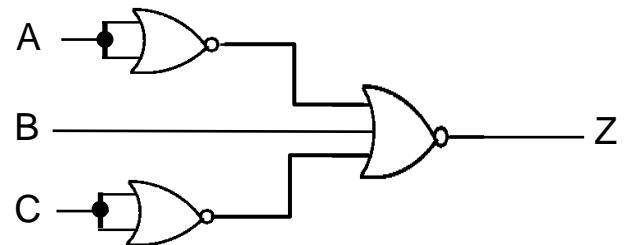
## ❑ Step 3:

- Assuming only NOR-gates available

$$Z = A \wedge \bar{B} \wedge C = \overline{\overline{A} \wedge \overline{\bar{B}} \wedge \overline{C}} = \overline{\overline{A} \vee \overline{\bar{B}} \vee \overline{C}}$$



## ❑ Function Minimization

- Boolean Algebra rules
- Karnaugh Method
- Quine McCluskey

# Logic Optimization

- ❑ Minimization: Step 2 b) Simplification → design the optimal circuit
  - ➡ Optimization problem with various cost functions
- ❑ The cost functions depends on design goals and the underlying technology
  - Common design goals
    - Monetary cost
      - Low amount of gates and connections, low number of input per gate
    - High speed
      - Parallel processing, low number of stages
    - Low power

# Case Study

- ❑ Combinational Adder: Design a circuit to perform the addition of 2 2-bit numbers

# Case Study

## ❑ Simplification

- $(A+B)(A+C) = ?$
- $A'BC + AB'C + A'BC + ABC' + ABC = ?$
  
- Consensus Theorem:  $AB + A'C + BC = AB + A'C$

# Digital Circuit Design Simplification

## ❑ Theorem: Absorption

$$a) x + (x \cdot y) = x$$

*Proof*

$$\begin{aligned} x + (x \cdot y) &= x \cdot 1 + x \cdot y \\ &= x \cdot (1 + y) \\ &= x \cdot 1 \\ &= x \end{aligned}$$

$$AB + A(B+C) + B(B+C)$$

$$b) x \cdot (x + y) = x$$

*Proof*

$$\begin{aligned} x \cdot (x + y) &= x \cdot x + x \cdot y \\ &= x + x \cdot y \\ &= x \end{aligned}$$

# Digital Circuit Design Simplification

□ Theorem:

$$a) x + (\bar{x} \cdot y) = x + y$$

*Proof*

$$\begin{aligned}x + (\bar{x} \cdot y) &= (x + \bar{x}) \cdot (x + y) \\&= 1 \cdot (x + y) \\&= x + y\end{aligned}$$

$$b) x \cdot (\bar{x} + y) = x \cdot y$$

*Proof*

$$\begin{aligned}x \cdot (\bar{x} + y) &= (x \cdot \bar{x}) + (x \cdot y) \\&= 0 + (x \cdot y) \\&= x \cdot y\end{aligned}$$

# Canonical Forms

- Definition (Literal): Boolean variable or complement of a Boolean variable

- Positive  $a$  Negative  $\bar{b}$

- Definition (Product term): AND- Operation on  $k \geq 1$  literals

$$a \quad ab\bar{c} \quad \bar{b}d \quad \bar{a}b\bar{c}d$$

- Definition (Sum term): OR-Operation on  $k \geq 1$  literals

$$b + \bar{d} \quad a + \bar{b} + c$$

- Definition (Minterm): Product term in which all variables appear exactly once (negated or non negated)

$$\bar{a}b\bar{c}d \quad abcd \quad \bar{a}\bar{b}\bar{c}\bar{d}$$

# Canonical- AND Normal Form

- **Definition (Maxterm):** Sum term in which all variables appear exactly one, negated or non negated

$$a + \bar{b} + c + d \quad a + b + c + d \quad \bar{a} + b + \bar{c} + \bar{d}$$

- **Theorem (Canonical Disjunctive Normal Form (CDNF)): Any Boolean function can be represented uniquely by a sum (OR) of minterms**

- From truth table, the CDNF is built by summing up all minterms for which the function value is 1
  - From a CDNF expression, built the function's truth table by entering a 1 in each function line corresponding to a minterm of the CDNF

# Canonical- AND Normal Form

- Theorem (Disjunctive Normal Form (DNF)), Sum of Products (SOP):  
Every Boolean Function can be represented as sum (OR-operation) of product terms
  - From the truth table: the DNF is constructed by summing (OR-ing) all minterms that for which the value of the function is 1
  - By simplification one can determine DNFs
- Implementation as 2-level circuit
  - Very fast, higher amount of gates

# Canonical- AND Normal Form

## ❑ Compact representation of the Boolean function

- Representation of minterms as code-word

$$m_5 = \bar{a}b\bar{c}d \quad m_8 = a\bar{b}\bar{c}\bar{d}$$

- Representation of a function as sum of all **minterm-Code-words**


$$\begin{aligned} \sum_{1}^n (8,7,3,1,11) &= m_8 + m_7 + m_3 + m_1 + m_{11} \\ &= a\bar{b}\bar{c}\bar{d} + \bar{a}b\bar{c}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}\bar{c}d + a\bar{b}cd \end{aligned}$$

# Canonical- AND Normal Form

## Function $z(a,b,c)$

$(i)_{10}$	$a$	$b$	$c$	$z$
0	0	0	0	1
1	0	0	1	1
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	0
7	1	1	1	1

## Corresponding Circuit

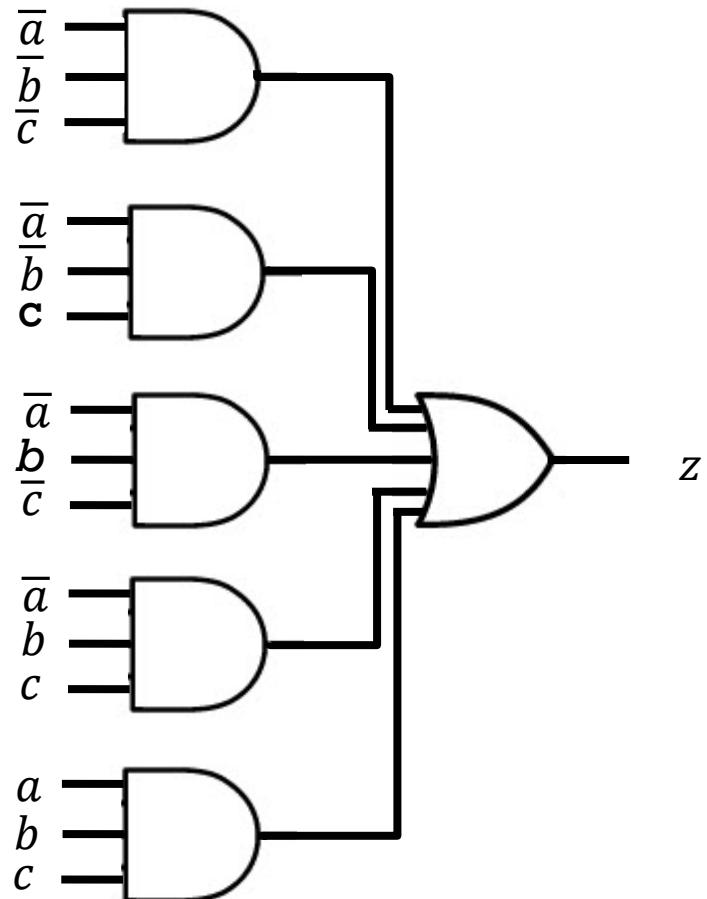

## Sum of minterms


$$\begin{aligned} z(a,b,c) &= m_0 + m_1 + m_2 + m_3 + m_7 = \\ &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + \bar{a}b\bar{c} + \bar{a}bc + abc \end{aligned}$$

# Canonical- AND Normal Form

□ Function  $z(a,b,c)$

$(i)_{10}$	$a$	$b$	$c$	$z$
0	0	0	0	1
1	0	0	1	1
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	0
7	1	1	1	1

□ Corresponding Circuit

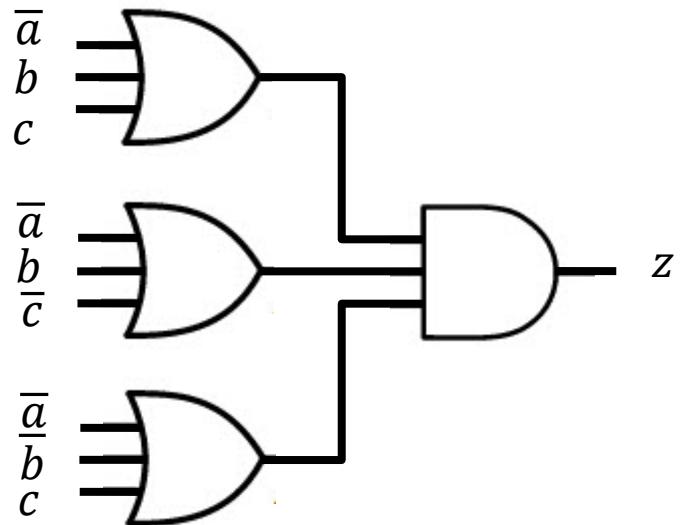

□ Product of Maxterms

$$\begin{aligned} z(a,b,c) &= M_4 \cdot M_5 \cdot M_6 = \\ &= (\overline{a} + b + c) \cdot (\overline{a} + b + \overline{c}) \cdot (\overline{a} + \overline{b} + c) \end{aligned}$$

# Logic Optimization

- Theorem: for a Boolean expression  $E$  and a variable  $x$  we have

$$Ex + E\bar{x} = E$$

- Proof:  $Ex + E\bar{x} = E(x + \bar{x}) = E$

- Applying this theorem reduces a SOP-form by one product term
  - The theorem is the basis of most optimization methods for 2-level logic

- Definition (Irredundant Sum): A SOP-form, that cannot be reduced by any product term anymore is call irredundant sum

# Logic Optimization Minimization Problems

- ❑ Minimization Problem: Given a function  $z(X)$ , compute a SOP-form  $E$  for  $z(X)$ , so that:
  1.  $E$  has a minimum number of product terms  
Necessary (but not sufficient condition).  $E$  is a irredundant sum
  2. Any other SOP-form  $E'$  of  $z(X)$  with a minimum number of product terms has at least the same number literals
- $E$  is called mimimal SOP

# Logic Optimization

## Implicant, prime implicant, Primfactors

- Definition (Implicant): An Implicant  $p$  of a function  $Z$  is a product term that fulfills the following :

$$\forall X : \quad p(X) = 1 \Rightarrow z(X) = 1$$

- $X$  is an assignment of the variables  $x_i$  (0/1)
  - Any minterm of  $p$  is also a minterm of  $Z$
  - An implicant can cover multiple 1s in the truth table of  $z$
- 
- Simplified definition: An implicant is a product term for which the value of the function is 1 in the truth table or in the Karnaugh-Map

# Logic Optimization

## Implicant, Prime implicant, Primfactors

- ❑ Definition(Prime implicant): An Implicant  $p$  of a function  $Z$  is called Prime implicant, if the removal of any literal from  $p$  does not result in an implicant of  $Z$
- Prime implicants are therefore no more reducible implicants of a function

# Logic Optimization

## Implicant, Prime implicant, Primfactors

❑ Example: The function  $z(a,b,c) = ab + bc + \bar{a}\bar{b}c$

has the following implicants:  $ab, bc, \bar{a}\bar{b}c$

but also:  $\bar{a}bc, ab\bar{c}, a\bar{b}c, abc$

prime implicants are only:  $ab, bc, ac$

a	b	c	z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# Logic Optimization

## Implicant, Prime implicant, Primfactors

Theorem: let  $E$  be a minimal SOP expression for a function  $z$ , then any product term of  $E$  is a prime implicant of  $z$

Proof through contradiction (Exercise)

In other words, the mimimal SOP expression is a sum of prime implicants

However, the theorem does not state which prime implicants must be selected

# Logic Optimization

## Mimimization Approach

- ❑ Minimization of 2-level logic functions in 2 steps:
  - Step 1: find all prime implicants
  - Find the minimum number of prime implicants, which cover all minterms of the function (covering problem).
    - If there are many possibilities, then chose the ones that produces the minimum number of literals (cost function)
  
- ❑ Minimization approach
  - Karnaugh-Map: graphical method, for very small cases (up to 5 variables)
  - Quine-McCluskey: tabular method, used to compute exact solution of the minimization problem (efficient on small number of variables)

# Logic Optimization

## Karnaugh Method– K-Map


- ❑ A Karnaugh-Map (K-Map) for a  $n$ -variable function is a special graphical representation of that function's truth table
  - $2^n$  cells, each of which corresponds to a row of the truth table
  - Each literal is associated with a row or a column
  - A cell has a unique address (numbering)
    - which is defined through cell-column/cell-row or
    - through a binary number, which is defined by literals in the column and row
  - Neighbor cells differs only on 1 position (bit) in their numbering
  - A K-Map is built by entering the value 1 in the address defined by the corresponding minterm from the truth table

# Logic Optimization

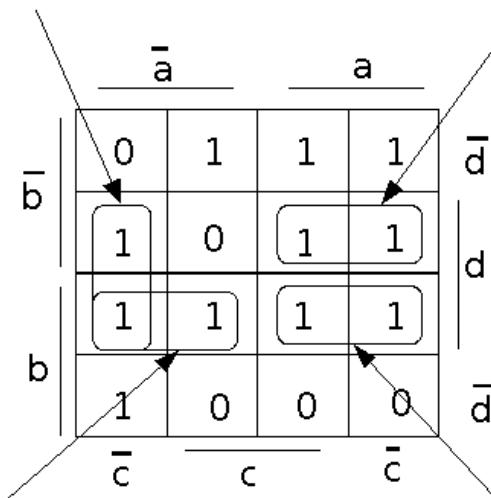
## Karnaugh Method– K-Map

- Cell arrangement insures that product terms with  $k$  literals are represented through rectangular blocks of  $2^{n-k}$  connected cells
  - $k=n \rightarrow$  Minterm  $\rightarrow$  1 cell
  - $k=0 \rightarrow$  Constant (0-Function, 1-Function)  $\rightarrow$  Block with all cells


$$\bar{a}\bar{b}\bar{c}d + \bar{a}b\bar{c}d = \bar{a}\bar{c}d$$



$$a\bar{b}cd + ab\bar{c}d = a\bar{b}d$$

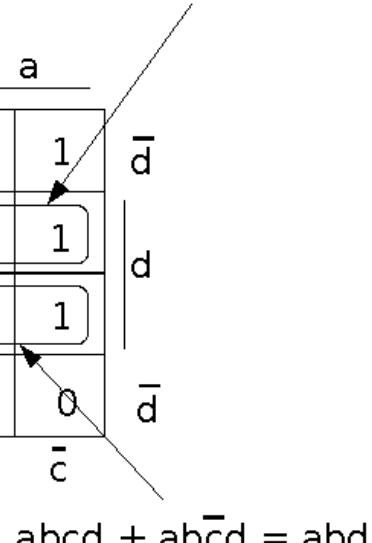
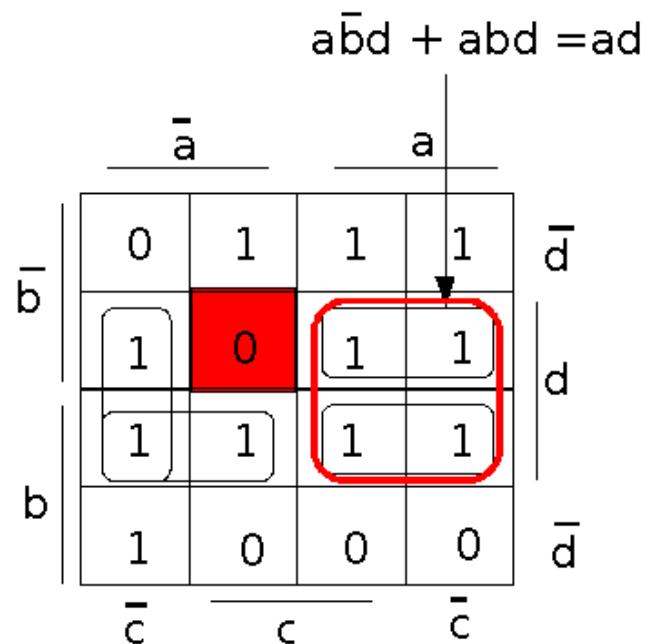
$$\bar{a}\bar{b}\bar{c}d + \bar{a}b\bar{c}d = \bar{a}bd$$




$$ab\bar{c}d + ab\bar{c}d = abd$$

# Logic Optimization

## Karnaugh Method– K-Map



### □ K-Map for n=2

a	b	z
0	0	0
0	1	1
1	0	1
1	1	0

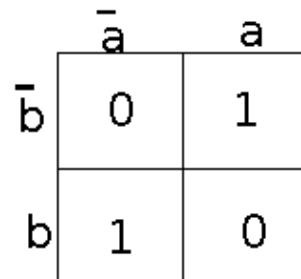

### □ K-Map for n=3

a	b	c	z
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

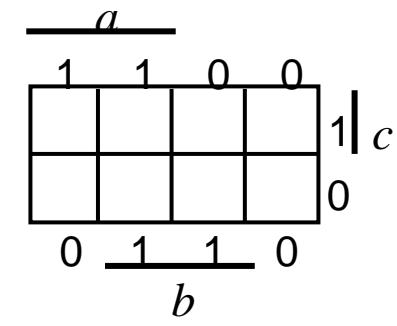
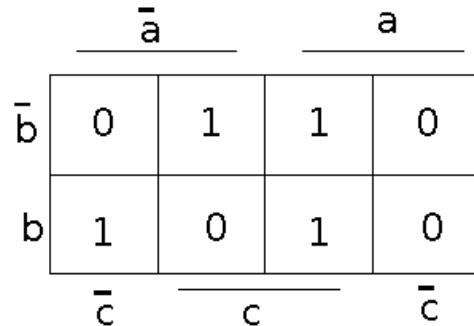


# Logic Optimization

## Karnaugh Method– K-Map

### □ K-Map for $n=4$

a	b	c	d	z
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

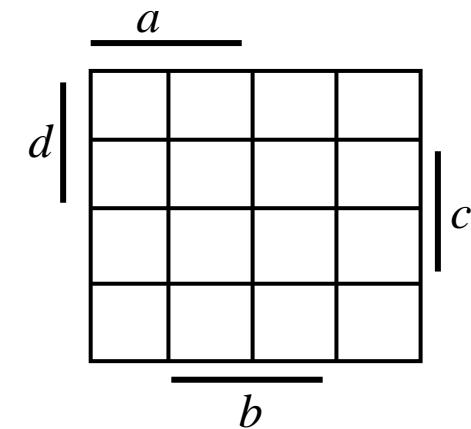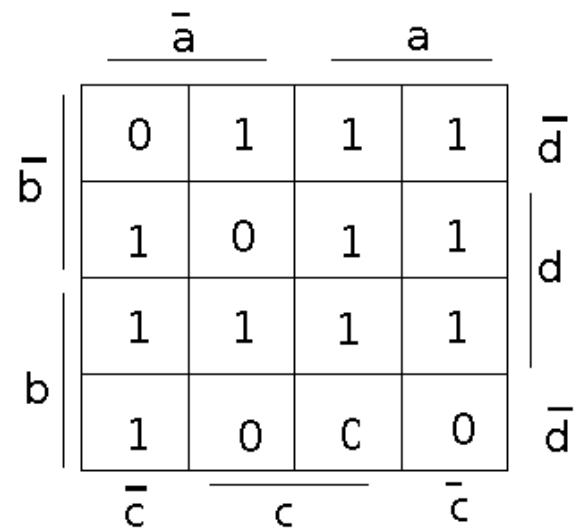

# Logic Optimization

## Karnaugh Method– K-Map

### □ Prime Implicant Examples

1	1	0	0
1	1	0	0

1	0	0	1
1	0	0	1

0	0	0	0
1	0	0	1
0	0	0	0

0	1	1	0
0	0	0	0
0	0	0	0
0	1	1	0

1	0	0	1
0	0	0	0
0	0	0	0

1	1	1	1
0	0	0	0
0	0	0	0
1	1	1	1

0	0	0	0
1	0	0	1

# Logic Optimization

## Karnaugh Method– K-Map

### ❑ Minimization with K-Map



1. Construct K-Map
2. Identify all prime implicants
  - prime implicants are rectangular blocks of  $2^{n-k}$  1's cells,  $0 \leq k \leq n$ , that are not contained in other blocks
  - prime implicants can overlap
3. Select a minimal number of prime implicants that covers all K-Map 1's
  - In case there are many alternatives, select the one with the minimum number of literals

# Logic Optimization

## Karnaugh Method– K-Map

### □ Example

a	b	c	d	z
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

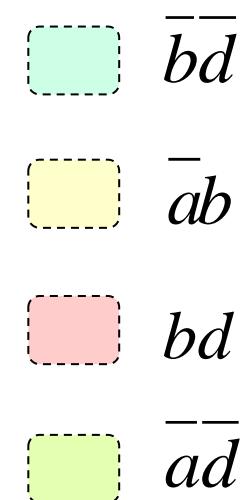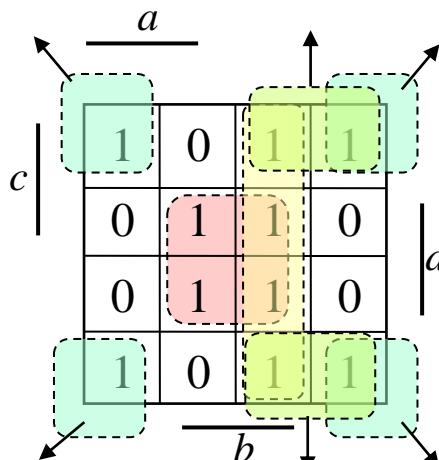

$$z = \bar{a}b + bd + \bar{b}\bar{d}$$


or

$$z = \bar{a}\bar{d} + bd + \bar{b}\bar{d}$$

# Logic Optimization
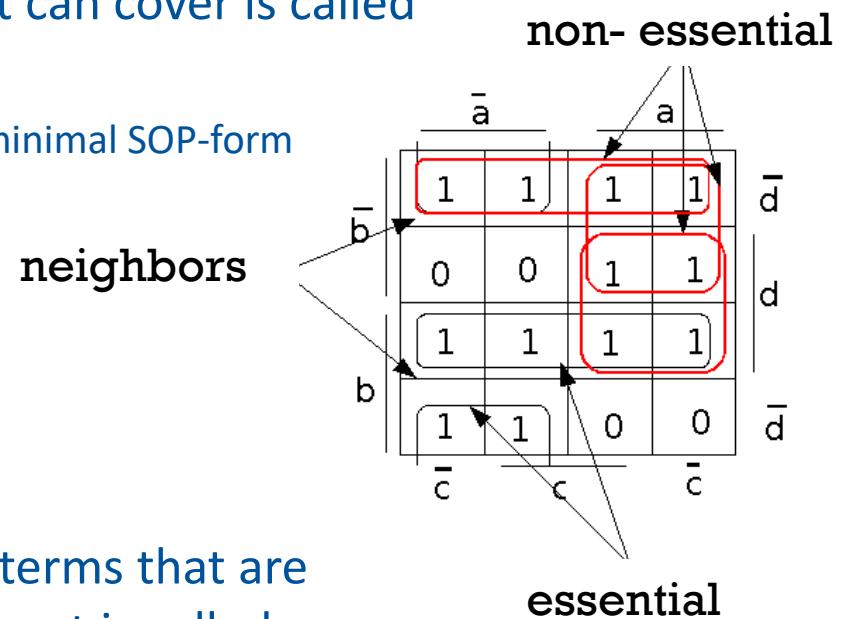
## Karnaugh Method– K-Map

- ❑ Definition (Essential prime implicant) A prime implicant that covers a minterm that no other implicant can cover is called essential prime implicant
  - Essential prime implicants must be part of any minimal SOP-form



- ❑ A prime implicant which only covers minterms that are already covered by essential prime implicant is called absolute non-essential
  - Non essential prime implicants should never be part of a minimal SOP

# Logic Optimization

## Karnaugh Method– K-Map


- ❑ How to select the non-essential prime implicants that will lead to the minimal SOP-Form ?
  - With K-Map, all possible combinations can be explored. The search space is usually not large
  - In realistic cases with more variables, computer-aided methods must be used. Efficient algorithms must be provided for efficient search

# Examples

<u>a</u>			
b			
	<u>c</u>		<u>d</u>
1	1	0	0
1	1	0	1
1	1	0	1
1	1	0	1

<u>a</u>	<u>b</u>	<u>c</u>	<u>d</u>	<u>z</u>
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

# 10-Min Quiz

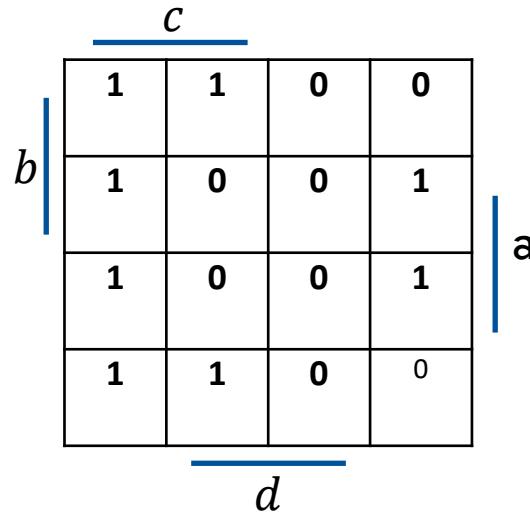

- ❑ Given the K-Map above for a function  $F$
- List 2 minterms of  $F$
  - List all prime implicants of  $F$
  - Does  $F$  has non-essential prime implicants ?
  - Compute the minimal Boolean expression of  $F$
  - Did you purchase the DAD Board?
    - If yes, from which vendor ?

# Logic Optimization

## Quine-McCluskey Algorithm

- ❑ Phase I: identification of Prime implicants
  1. Make a list  $L_1$  of all minterms, sorted in groups  $G_h$ ,  
 $0 \leq h \leq n$ , where  $G_h$  consists of all minterms with  $h$  '1's in their code-word
  2. Using list  $L_i$  compare all elements  $E'$  in  $G_h$  with  $E''$  in  $G_{h+1}$ .  
if  $E' = Ex$  and  $E'' = E\bar{x}$ , apply the minimization theorem, mark  $E'$  and  $E''$ , and insert  $E$  in the group  $G_h$  of a new List  $L_{i+1}$ , if not yet included
  3. If  $L_{i+1}$  is not empty, set  $i = i + 1$  and go to step 2.  
if  $L_{i+1}$  is empty, then the non-marked inputs  $L_1, \dots, L_i$  are prime implicants

# Logic Optimization

## Quine-McCluskey Algorithm

$$z(a,b,c,d) = \sum(1, 3, 5, 10, 11, 12, 13, 14, 15)$$

 $L_1$  $L_2$  $L_3$ 

The diagram illustrates the Quine-McCluskey algorithm's iterative process:

- Step 1 ( $L_1$ ):** Prime implicants are grouped by their number of 1s. Red checkmarks indicate which minterms are included in each group.
 

Group 1	$m_1 = 0001$	✓
Group 2	$m_3 = 0011$	✓
	$m_5 = 0101$	✓
	$m_{10} = 1010$	✓
	$m_{12} = 1100$	✓
Group 3	$m_{11} = 1011$	✓
	$m_{13} = 1101$	✓
	$m_{14} = 1110$	✓
Group 4	$m_{15} = 1111$	✓
- Step 2 ( $L_2$ ):** Implicants are grouped by the number of 1s they share with the previous row. Red checkmarks indicate which minterms are included in each group.
 

Group 1	00-1 0-01	✓
Group 2	-011 -101 101-	✓
Group 3	11-0 110- 1-10	✓
- Step 3 ( $L_3$ ):** The final result table shows the prime implicants.
 

Group 2	1-1- 11--
---------	--------------

Prime implicants:

$$\{P_A, P_B, P_C, P_D, P_E, P_F\} = \{00-1, 0-01, -011, -101, 1-1-, 11--\}$$

# Logic Optimization

## Quine-McCluskey Algorithm

- ❑ Phase II: Compute the minimum sum of all prime implicants
  1. Make a coverage table T in which rows represent prime implicants and columns minterms. Mark all cells  $T_{i,j}$  in the table with X, if the prime implicant in row i covers minterm of column j
  2. Identify all essential rows of T and insert the corresponding prime implicants to the solution. Reduce T by erasing the essential row and all columns that are covered by the row. Reduce T further by erasing dominant column and dominant rows
  3. Apply step 2 until T cannot be further reduced. If T is empty, then solution is S. If not, go to step 4
  4. Apply distributive law to compute a minimal SOP-form for the remaining rows of T

# Logic Optimization

## Quine-McCluskey Algorithm

- Coverage table example

	$m_1$ 0001	$m_3$ 0011	$m_5$ 0101	$m_{10}$ 1010	$m_{II}$ 1011	$m_{I2}$ 1100	$m_{I3}$ 1101	$m_{I4}$ 1110	$m_{I5}$ 1111
$P_A = 00-1$	X	X							
$P_B = 0-01$	X		X						
$P_C = -011$		X			X				
$P_D = -101$			X				X		
$P_E = 1-1-$				X		X		X	X
$P_F = 11--$						X	X	X	X

essential  
essential

$$S = \{P_E, P_F\}$$

# Logic Optimization

## Quine-McCluskey Algorithm

- ❑ Row dominance: Row  $P_i$  dominates row  $P_j$ , if  $P_i$  has X in any column in which  $P_j$  also has X
  - Either  $P_i$  has more X than  $P_j$ , or  $P_i = P_j$
  - A dominant row covers the same or more minterms than the dominated row
- A dominated row can be removed from the coverage table, if it contains more literals than the dominant row
  - Random choice if  $P_i = P_j$  and the two rows have the same number of literals

X	X	X	X	$p_1$	$q_1$	
	X		X	$p_2$	$q_2$	
						...
X		X	X	$p_k$	$q_k$	

X	X	X	X	$p_1$	$q_1$	
	X		X	$p_2$	$q_2$	
						...
X		X	X	$p_k$	$q_k$	

# Logic Optimization

## Quine-McCluskey Algorithm

- ❑ Column dominance: Column  $m_i$  dominates  $m_j$ , if  $m_i$  has X in any row in which  $m_j$  also has X
  - A dominant column can be erased, since every coverage of  $m_j$  is also a coverage of  $m_i$
  - choose any to erase, if the two columns are identical

	$m_i$	$m_j$
$p_1$	X	X
$p_2$		
$p_3$	X	X
$p_4$	X	
$p_5$	X	

	$m_i$	$m_j$
$p_1$	X	X
$p_2$		
$p_3$	X	X
$p_4$	X	
$p_5$	X	

- $p_1$  and  $p_3$  cover  $m_i$  and  $m_j$ :  $p_4$  and  $p_5$  are redundant in regard to  $m_i$  and  $m_j$

# Logic Optimization

## Quine-McCluskey Algorithm

	$m_1$ 0001	$m_3$ 0011	$m_5$ 0101
$P_A = 00-1$	X	X	
$P_B = 0-01$	X		X
$P_C = -011$		X	
$P_D = -101$			X

$P_A$  dominates  $P_C \rightarrow$  erase  $P_C$   
 $P_B$  dominates  $P_D \rightarrow$  erase  $P_D$

$P_A = 00-1$   
 $P_B = 0-01$

	$m_1$ 0001	$m_3$ 0011	$m_5$ 0101
	X	X	

$m_1$  dominates  $m_3, m_5$   
 $\rightarrow$  erase  $m_1$

	$m_3$ 0011	$m_5$ 0101
	X	

$$S = \{P_E, P_F, P_A, P_B\} =$$

$$\{00-1, 0-01, 1-1-, 11--\} =$$

$$\overline{ab}d + \overline{ac}d + ac + ab$$

$P_A, P_B$  are essential

$P_A = 00-1$   
 $P_B = 0-01$

# Logic Optimization

## Quine-McCluskey Algorithm

- Branching
  - If the coverage table  $T$  still has  $k$  rows and cannot be further reduced, randomly chose a row  $P_i$  and „tentatively“ insert the corresponding prime implicant to the solution  $S$ . Erase  $P_i$  and all columns covered by  $P_i$ . Further reduce  $T$  by erasing new resulting essential rows, dominant columns and dominated rows
  - If the coverage table becomes empty, note the tentative solution  $S$ , and repeat the process for all remaining  $k-1$  row. The final solution is the one with the lowest cost among the tentative  $k$  solutions
  - If the coverage table is not empty, select another  $P_j$  and proceed as described above. In worst-case, the algorithm will result in an exponential run-time



Herbert Wertheim  
College of Engineering  
UNIVERSITY *of* FLORIDA