

## Problem 2

3 state bits ; 3 output bits

$Q_2 Q_1 Q_0$	$Q_2^+ Q_1^+ Q_0^+$	$D_2 S_1 R_1 J_0 K_0$	$Q_{out}$
0 0 0	0 0 1	0 0 x 1 x	0 0 1
0 0 1	0 1 0	0 1 0 x 1	0 1 1
0 1 0	0 1 1	0 x 0 1 x	0 1 0
0 1 1	1 0 0	1 0 1 x 1	1 1 0
1 0 0	1 0 1	1 0 x 1 x	1 1 1
1 0 1	0 0 0	0 0 x x 1	1 0 1
1 1 0	x x x	x x x x x	x x x
1 1 1	x x x	x x x x x	x x x

$D_2:$

$Q_2 Q_1$	$Q_0$	
0 0	0 1	0 0
0 1	0 1	0 1
1 1	0 1	x x
1 0	0 1	1 0

$Q_0 Q_1$   $\bar{Q}_0 Q_2$

$$D_2 \leq \bar{Q}_0 Q_2 + Q_0 Q_1$$

$S_1:$

$Q_2 Q_1$	$Q_0$	
0 0	0 1	0 1
0 1	0 1	x 0
1 1	0 1	x x
1 0	0 1	0 0

$\sim \bar{Q}_2 \bar{Q}_1 Q_0$

$$S_1 \leq \bar{Q}_2 \bar{Q}_1 Q_0$$

$R_1:$

$Q_2 Q_1$	$Q_0$	
0 0	0 1	x 0
0 1	0 1	0 1
1 1	0 1	x x
1 0	0 1	x x

$Q_1 Q_0$

$$R_1 \leq Q_1 Q_0$$

$J_0:$

$Q_2 Q_1$	$Q_0$	
0 0	0 1	1 x
0 1	0 1	1 x
1 1	0 1	x x
1 0	0 1	1 x

1

$$J_0 \leq 1 (V_{cc})$$

$$K_0 \leq 1 (V_{cc})$$



Out<sub>2</sub>:

$q_2 q_1$	0	1
00	0	0
01	0	1
11	X	X
10	1	1

Out<sub>1</sub>  $\angle = q_1 q_0 + q_2$

Out<sub>1</sub>:

$q_2 q_1$	0	1
00	0	1
01	1	1
11	X	X
10	1	0

Out<sub>1</sub>  $\angle = q_1 + (q_2 \oplus q_0) \cdot 0$

Out<sub>0</sub>:

$q_2 q_1$	0	1
00	1	1
01	0	0
11	X	X
10	1	1

Out<sub>0</sub>  $\angle = \bar{q}_1$

