

VHDL-Overview

Christophe Bobda

VHDL

VHDL: **V**ery high speed integrated circuits **H**ardware **D**escription **L**anguage

~~Very Hard Design Language~~

Hardware-Description Language with the goals

Simulation

IC synthesis


Description is done under the aspects

Behavior

Structure


Hierarchy

Parallelism

 

Only synthesizable Subset is considered !

 Entity – Wrapper and interface definition




logic encapsulation of a unit Interface

Definition: **Port** \rightarrow X


Port are defined through **Identifier**,
Direction und **Data-type**

Direction: **in**, **out**, **inout**, **buffer**

Data-type: bit, std_logic(_vector), ADT

 

View from outside

 

View from inside

Signals can be connected
to ports from inside or from
outside.


Entity as „Black Box“

Viewed from outside an entity is a „black box“

→ The structure and behavior (functionality) is hidden

Example below: Entity with two inputs and one output port

Functionality not defined yet

 

Entity – Definition

Keywords in blue

Library to be used

Which part of the library should be

Prefix

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

Entity-Definition

```
ENTITY two_gate IS
```

Interface

```
PORT ( x1, x2 : IN std_logic;  
       y      : OUT std_logic );
```

```
END two_gate;
```

Name of the Entity

Output-Signal with name: y

Data-type of the signal
(multi-value logic)


VHDL is case insensitive !

Architecture – Behavior of the Entity

The behavior of an Entity is described in the **Architecture**.

The Architecture

 - has a unique name,
- signals and components can be internally declared,
- is assigned to a unique Entity.




```
ARCHITECTURE <Architecture name> OF <Entity-Name> IS  
[Declarations]  
BEGIN  
    [Architecture Statements]  
END <Architecture name>;
```

Architecture – Example

NAND-Gate

based on the previous Entity-Definition:

 

Signal assignment

Architecture name

Entity name

```
ARCHITECTURE two_gate_nand OF two_gate IS  
BEGIN
```

```
    y <= NOT ( x1 AND x2 );
```

```
END two_gate_nand;
```

Behavioral description:

one statement with pre-defined and
pre-implemented functions: AND, OR, NOT

Architecture name

XOR-Entity

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY xor_gate IS
```

```
PORT( x1, x2  : IN    std_logic;
```

```
      y       : OUT   std_logic );
```

```
END xor_gate;
```

```
ARCHITECTURE behavioral OF xor_gate IS
```

```
BEGIN
```

```
    y <= x1 XOR x2;
```

```
END behavioral;
```


VHDL Operators

Signal Assignment: $y \leq x1$

Boolean Operators:

- **AND/and:** logical and
- **OR/or:** logical or
- **NAND/nand:** logical complement of and
- **NOR/nor:** logical complement
- **XOR/xor:** logical exclusive
- **XNOR/xnor:** logical complement of exclusive

Random Boolean statement can be specified in VHDL.
Use parentheses to enforce precedence

$y \leq (x1 \text{ XOR NOT}(x2 \text{ XOR } X3)) \text{ NAND } y;$

Process – Parallel statements

VHDL describes parallel processes

- All signal assignments take place simultaneously

<u>VHDL</u>		<u>JAVA</u>
A <= B;	=	C <= D;
C <= D;		A <= B;

<u>VHDL</u>		<u>JAVA</u>
A <= B;	≠	A = B;
C <= A;		C = A;

Example

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY my_circuit IS

PORT( a, b      : IN      std_logic;
      x, y, z    : OUT    std_logic );
END my_circuit ;

ARCHITECTURE behavioral OF my_circuit IS
BEGIN
    y <= a XOR (a AND NOT(b));
    z <= b OR NOT b;
    x <= b OR NOT b;
END behavioral;
```

Design Flow

Modern design is done using CAD (computer-aided design) or EDA (Electronic Design Automation) tools

- FPGA: Xilinx Vivado, Intel Quartus
- VLSI: Synopsys DC, Cadence,

Design Flow: Lab1 will take you through the steps

- Design Entry
- Functional Simulation
- Synthesis (Pins and Library assignment, compilation)
- Post-synthesis simulation (timing analysis, verification)
- Place and Route (Layout)
- Fabrication/Bitstream Download (FPGA)

Signals

- A signal defines a **connection in hardware**. Can be used to connect components within an entity
- A signal has a **datatype**, which is the of possible values + operations on those values
- Signal Declaration

SIGNAL *signal_name1[, signal_name2, ...] : signal_type;*

- Declaration can be done in
 - Package
 - Port-section of an entity
 - Declaration section of an entity
- Signal Assignment is performed with symbol <=
a <= b xor c

Internal Signals

ENTITY Position IS

PORT(A : in std_logic_vector(**2 downto 0**);
B : out std_logic_vector(0 to 2));

END Position;

ARCHITECTURE behv OF Position IS

SIGNAL signal1, signal2: std_logic;

SIGNAL signal3 : std_logic_vector(4 **downto** 0);

Begin

signal1 <= A(0) **AND** B(2);

B(0) <= signal1 **XOR** A(1);

...

Variables

- A variable defines a **memory location**. Can be used to store values.
- A variable has a **datatype**, which is the set of all possible values + operations on those values
- Variable Declaration

VARIABLE *var_name1[, var_name2, ...] : variable_type;*

- Declaration can be done **exclusively in a process**
- Variable assignment is performed with symbol **:=**
a := b xor c

```
PROCESS(a, b)
  VARIABLE c: bit;

  c := b and c;
```

Datatypes

Datatype

- Define a **set of values** a signal or a variable can take, along with operations on those values.
- Predefined datatype
 - bit (std_logic): '0', '1'
 - bit_vector (std_logic_vector): "00101", "001001"
 - integer: 10, 123, 56
 - character: 'a', 'v', 'n'
 - string: "anmggzem"
 - Boolean: FALSE, TRUE
 - real: 1.23, 234.6, -0.34
- User-defined datatype
 - SATES
 - CAN_PARAMETERS
 - NETWORK_PACKET
 - ...

Multi-Value Logic


- Standard logic IEEE 1164
 - Declaration in Package „standard_logic_1164“
 - Possible values:
 - ‘U’ not initialized
 - ‘X’ unknown
 - ‘0’ Logic 0
 - ‘1’ Logic 1
 - ‘Z’ high impedance
 - ‘W’ unknown (weak signal)
 - ‘L’ logic 0 (weak signal)
 - ‘H’ Logic 1 (weak signal)
 - ‘-’ Don't care
 - Standard_logic_vector: Vektor von standard_logic values

Bit vectors

Single signals can be grouped in a vector:

`std_logic` \rightarrow `std_logic_vector()`

Example: 3-bit coded position

 


ENTITY Position IS

PORT(A : in std_logic_vector(**2 downto 0**);

B : out std_logic_vector(0 to 2));

END Position;

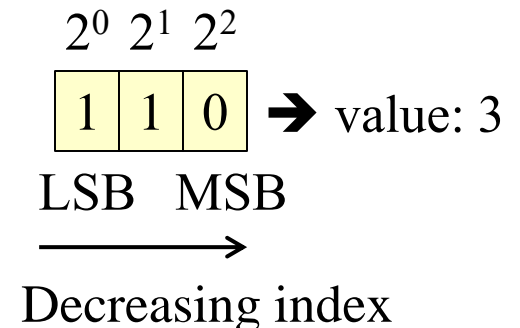3-bit wide, binary coded Bit-vector,
write: x **downto** y means decreasing index from
the MSB to the LSB
(MSB: most significant bit, LSB: least ...)



Bit Vectors

- Declaration
 - `signal Z_Bus: bit_vector(3 downto 0);`
 - `signal Z_Bus: std_logic_vector(0 to 3);`
- Assignment:
 - “By position”
 - `Z_Bus(3) <= C_Bus(1);`
 - `Z_Bus(1) <= C_Bus(1);`
 - `Z_Bus(3 downto 2) <= “01”`
 - “Concatenation”:
 - `Z_Bus <= A & B & C & D;`
 - “Aggregates”:
 - `Z_Bus <= (A, B, C, D);`
 - “Specifying by element index”:
 - `Z_Bus <= (3 => ‘ 1’, 1 downto 0 => ‘ 1’, 2 => ‘ 0’);`
 - “others”:
 - `Z_Bus <= (3 => ‘ 1’, 1 => ‘ 0’, other => ‘ 0’);`


VHDL Operators

- Logic operators
 - AND, OR, NAND, NOR, XOR (equal precedence)
 - NOT (higher precedence)
- comparison
 - < (smaller than), <= (smaller or equal than), = (equal), >= (bigger or equal) , > (bigger than), /= (different)
- Arithmetic operators
 - + (Addition), - (subtraction), * (Multiplication), / (Division), ** (Exponent), abs (Magnitude), mod (Modulo), rem (Remainder)

Process – Parallel statements


Process execution:

 - Section (module) in the architecture where **instructions execute sequentially**
- Multiple processes in same architecture execute in parallel
- Processes communicate with other components using signals
- A process has a sensitivity list. That is the list of all signals that activate the process when their value change (**event**)



Process – Declaration

Syntax of a process declaration

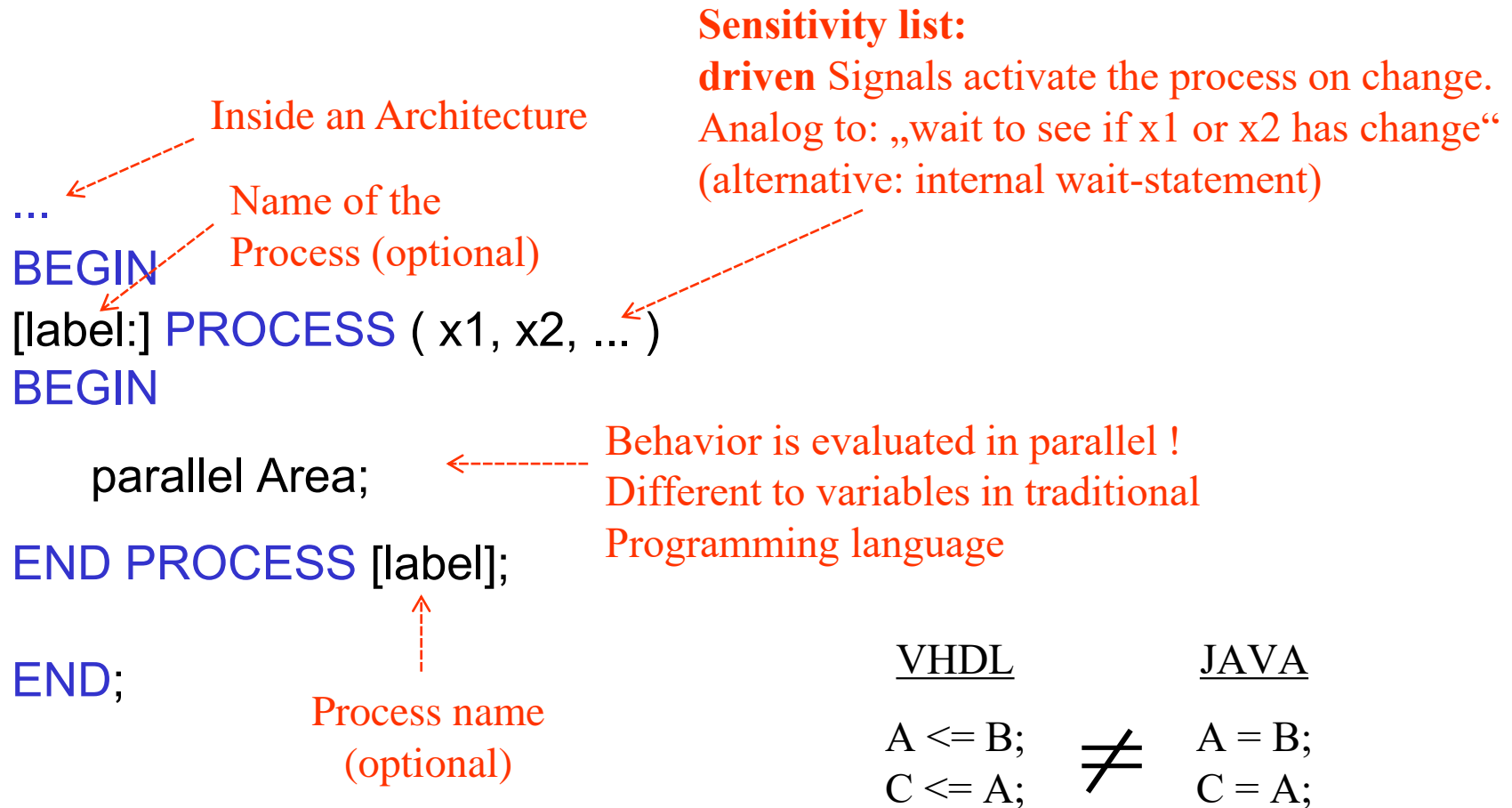

Process – Example

Entity Or is

port (A, B: **in bit**;
Z: **out bit**);

End or;

Architecture Behave of or is

Begin

-- process declaration

or_func:process (A,B)

-- A, B in the sensitivity list

begin

if (A = '1' or B = '1') **then**


Z <= '1' ;

Else

Z <= '0' ;

End If;

End Behave;

 

Control-flow

Branching

If and If - then - else – syntax

```
If condition 1 then  
    sequential instructions
```

```
End if;
```

```
If condition 2 then  
    sequential instructions
```

```
End if;
```

```
If condition 3 then  
    sequential instructions
```

```
End if;
```

```
If condition 4 then  
    sequential instructions
```

```
Else
```

```
    sequential instructions
```

```
End if;
```

If - elsif – syntax

```
If condition 1 then  
    sequential instructions
```

```
elsif condition 2  
    sequentielle instructions
```

```
elsif condition 3  
    sequential instructions
```

```
else  
    sequential instructions
```

```
End if;
```


Control-flow

Branching

```
Case Object is
  when value 1 => instructions
  when value 2 => instructions
  .....
  when value n => instructions
End case;
```

```
Interval differentiation
Case X is
  when 0 to 2 => instructions
  when value 1 => instructions
  .....
  when value n => instructions
End case;
```

```
Subset differentiation
Case X is
  when 0 to 2 => instructions
  when value 1 => instructions
  .....
  when value n => instructions
  when others => instructions
End case;
```

Control-flow

Branching

IF – THEN – ELSE

CASE

(**y** of type **std_logic**: 1, 0, Z, X, ...)

```
LOGIC : PROCESS ( x1, x2, x3 )  
BEGIN
```

```
  IF ( x1 = '1' ) THEN
```

```
    y <= '0' ;
```

```
  ELSIF ( x2 = '1' ) THEN
```

```
    y <= '1' ;
```

```
  ELSE
```

```
    y <= 'Z' ;
```

```
  END IF;
```

```
...
```

```
...
```

```
CASE x3 IS
```

```
  WHEN '0' =>
```

```
    y <= '0' ;
```

```
  ...
```

```
  WHEN others =>
```


```
    y <= '1' ;
```

```
END CASE;
```

```
END PROCESS LOGIC;
```

Default case

Not elseif

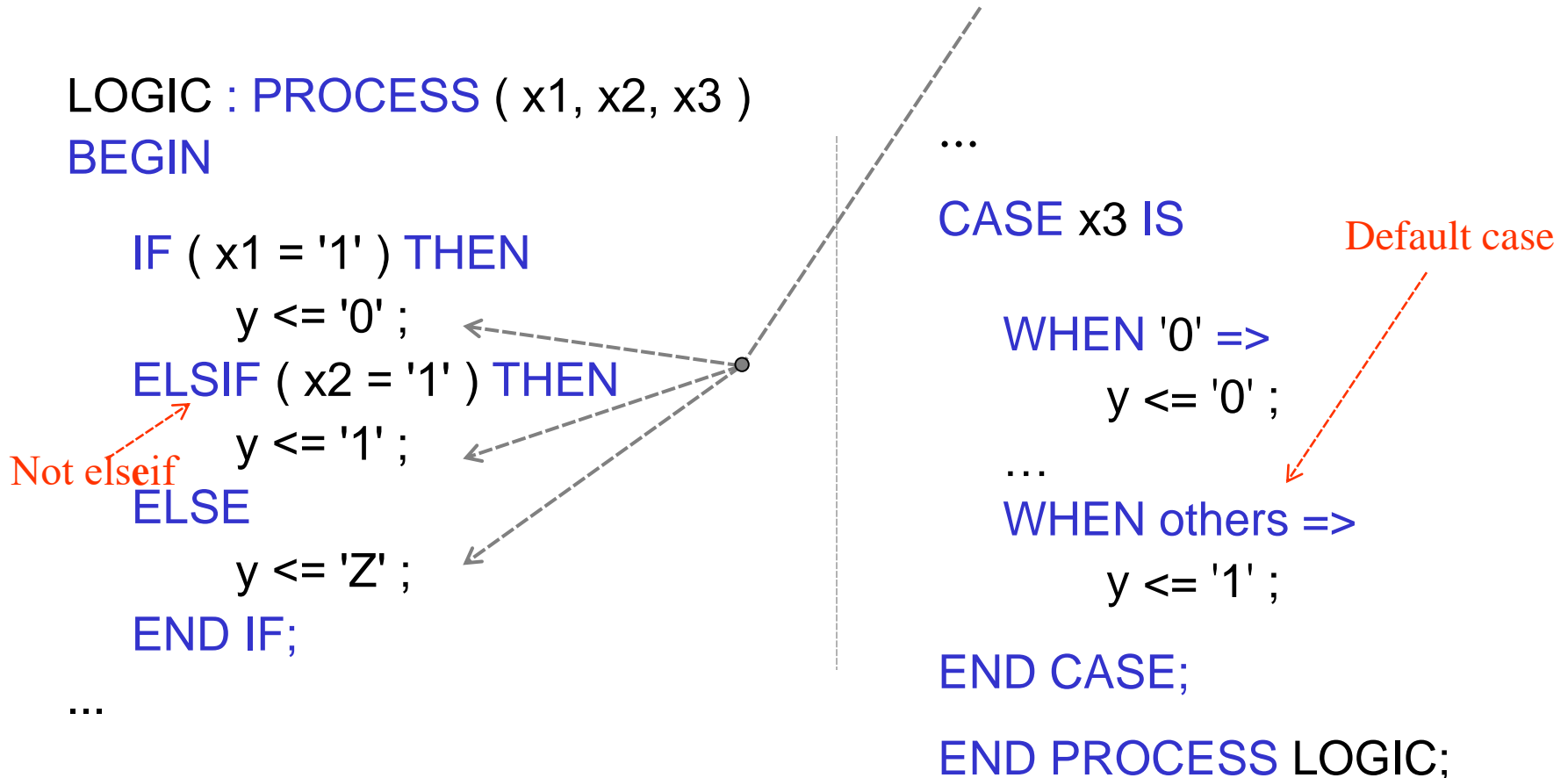


Synchronous Circuits

Synchronous circuits: outputs are correct with the value of the clock

Clock: special signal with alternating 1 and 0 values

Clock Cycle: Distance between two edge

Edges can be positive or negative

 

VHDL: Positive edge

`((clock'event) AND (clock = '1'))`

VHDL: negative edge

`((clock'event) AND (clock = '0'))`


Hierarchy

Hierarchy (**structural description**)


- Components (modules, submodules) are instantiated in a high level (top level) design to build more complex structures
- **Example: Full Adder**
 - Instantiation of 2 half adders and 1 XOR-Gate

In the same or separate files
of the same project

Name file after the entity

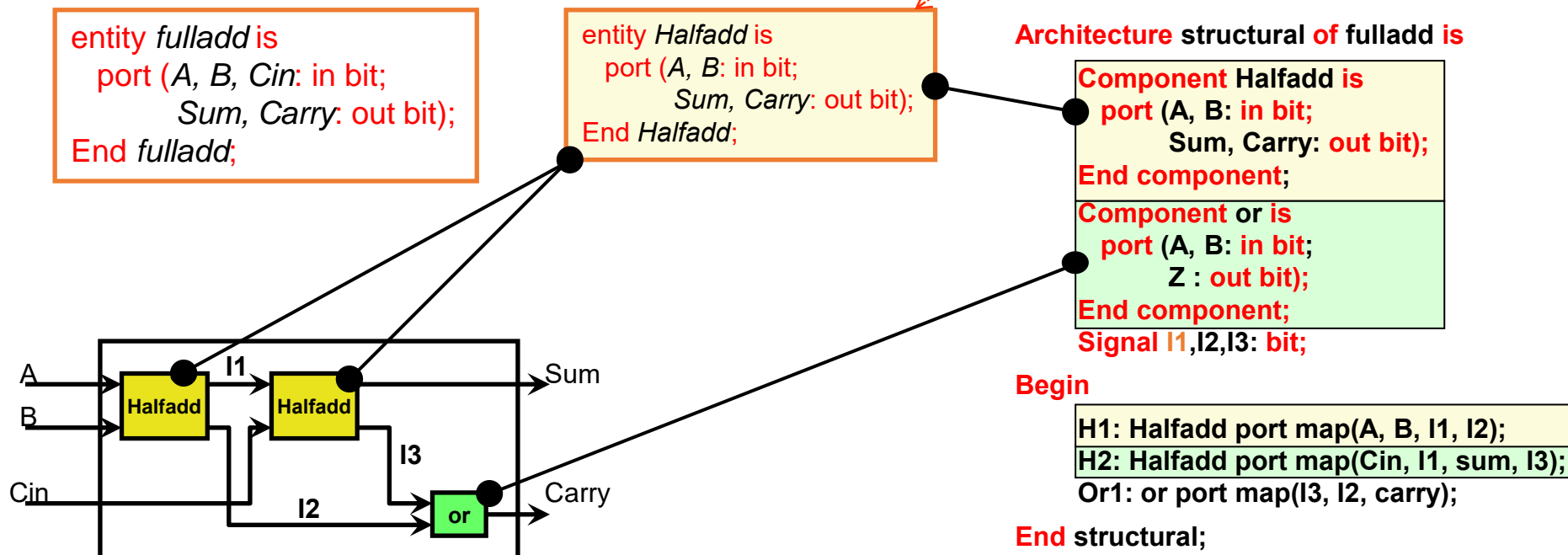

Use of components

 


Example: XOR

Structural description

Ports: 2 inputs and 1 output

Reuse of **two_gate**, here with names **ent1**, **ent2** and **ent3**

xor

 

Components

ent1, ent2 (AND-Gate)

ent3 (OR-Gat)

inv1, inv2 (Inverter)

XOR-Entity

Entity-Declaration

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY xor_gate IS  
  
    PORT( x1, x2    : IN    std_logic;  
          y         : OUT   std_logic );  
  
END xor_gate;
```

XOR – Components Declarations

Architecture-Declaration

Use of pre-implemented components

```
ARCHITECTURE xor_behavior OF xor_gate IS
```

```
    COMPONENT and_gate
```

```
        PORT ( x1, x2: in std_logic; y: out std_logic );
```

```
    END COMPONENT;
```

```
    COMPONENT or_gate
```

```
        PORT ( x1, x2: in std_logic; y: out std_logic );
```

```
    END COMPONENT;
```

```
    SIGNAL connect1, connect2: std_logic;
```

```
    SIGNAL inv1, inv2: std_logic;
```

```
BEGIN
```

```
...
```


XOR – Components Instantiation

Instantiation and component wiring

Type of the Instance Wiring: **Internal** => **External**

```
...  
ent1: and_gate PORT MAP (x1 => x1,      x2 => inv1,      y => connect1 );  
ent2: and_gate PORT MAP (x1 => inv2,     x2 => x2,        y => connect2 );  
ent3: or_gate  PORT MAP (x1 => connect1, x2 => connect2, y => y );  
...
```


Instance

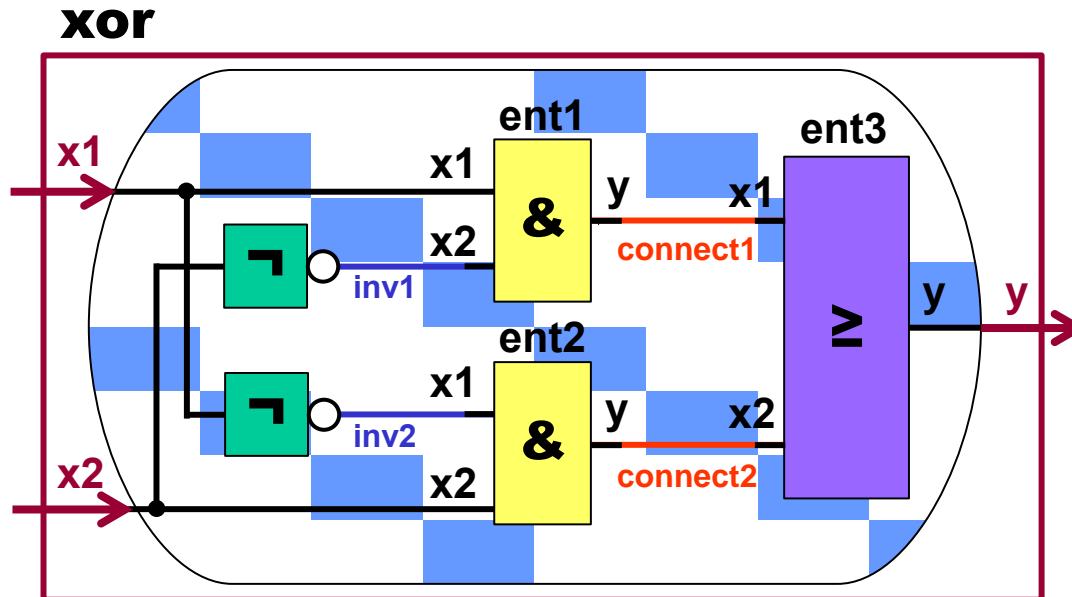

XOR- Component Wiring


ent1: two_gate

```
PORT MAP ( x1 => x1,  
           x2 => inv1,  
           y  => connect1 );
```

 


ent2: two_gate

```
PORT MAP ( x1 => inv2,  
           x2 => x2,  
           y  => connect2 );
```

 

ent3: two_gate
 
```
PORT MAP ( x1 => connect1,  
           x2 => connect2,  
           y  => y );
```



Line break is not required !!

XOR-Architecture


Inversion of the input-signals

```
...  
INV : PROCESS ( x1, x2 )  
BEGIN  
    inv1 <= NOT x2;  
    inv2 <= NOT x1;  
END PROCESS INV;  
  
END xor_arch;
```

Process name



Sensitivity-List

Assignment of the inverted input-signals

 

Automata - Finite State Machine

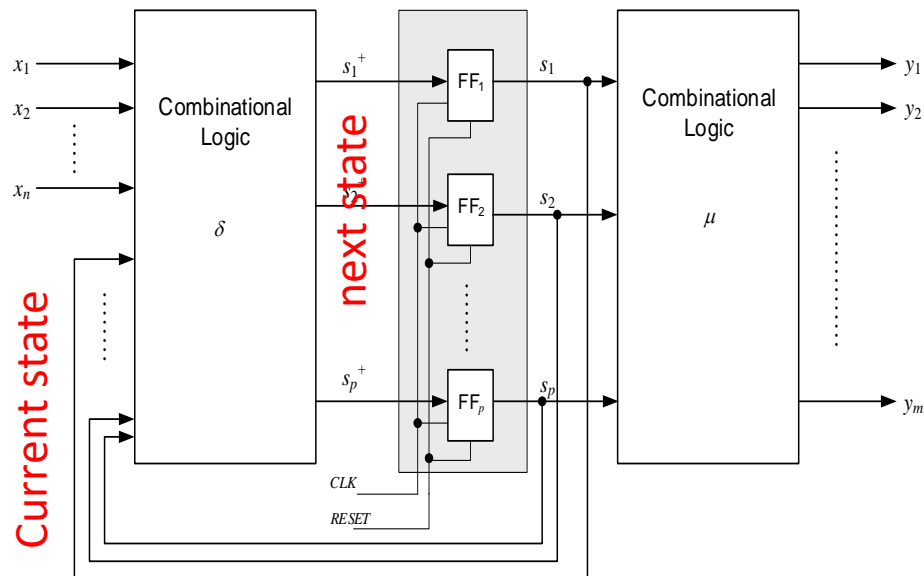 Combinational block + Sequential (Mealy or Moore)



Automata - Finite State Machine

- Combinational block + Sequential (Mealy or Moore)
- 2 different processes

```
TYPE state_type IS ( S0, S1 ) ;  
SIGNAL current_state, next_state: state_type ;  
  
Comb : PROCESS ( current_state )  
BEGIN  
    CASE current_state IS  
        WHEN S0 =>  
            next_state <= S1 ; ...  
        WHEN others =>  
            next_state <= S0 ; ...  
    END CASE;  
END PROCESS Comb;
```


Definition of the state vector

This will connect the input and output of your FF

Set the next state

Here also output !!

Default case

 

...

Automata - Finite State Machine

- Next-State-Assignment in a separate process
- Asynchronous Reset → Reset to state „S0“ (initial state)
- Synchronous state transition on rising edge of the Clock-Signal „CLK“

...

```
Synch : PROCESS ( CLK, RESET )
```

```
BEGIN
```

```
    IF ( RESET = '1' ) THEN -- define an asynchronous reset
```

```
        CURRENT_STATE <= S0;
```

```
    ELSIF ( CLK'EVENT and CLK = '1' ) THEN
```


```
        CURRENT_STATE <= NEXT_STATE;
```

```
    END IF;
```

```
END PROCESS Synch;
```

rising CLK-edge


State transition

 

Functional Simulation


Used to check functional correctness of the circuit

 - A testbench consist of the design under test (DUT) and the framework to generate **stimuli** and verify result
 - The correctness of the circuit is verified in a "**Waveform-Viewer**"



Testbench-Entity

 Empty wrapper which instantiates the entity under test



```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
ENTITY my_tb IS
```

```
END my_tb ;
```

No Port-Definition

Name of the Testbench

Testbench-Architecture

- Declaration of the component under test
- Local signal to connect the component under test
- Signals and ccomponents declaration at the beginning of the architecture

```
ARCHITECTURE my_tb_behavior OF my_tb IS
    SIGNAL tb_x1, tb_x2, tb_y : std_logic;
    COMPONENT
        xor_gate PORT ( x1, x2 : in std_logic; y: out std_logic );
    END COMPONENT;
BEGIN
    ...
```

Annotations:

- Name of the Testbench-Architecture (points to `my_tb_behavior`)
- Name of the Testbench (points to `my_tb`)
- Three local Signals (points to `tb_x1, tb_x2, tb_y`)
- Declaration of the component under test (points to `xor_gate`)
- Type of the component (points to `PORT`)
- Interface Definition (points to `PORT (x1, x2 : in std_logic; y: out std_logic);`)

Testbench-Architecture

Instantiation and component wiring

Component instantiation


```
...  
BEGIN  
    test_ent : xor_gate  
        PORT MAP (x1 => tb_x1, x2 => tb_x2, y => tb_y);  
...  
my_tb
```

Component's type

Component-Port

local signal

wiring:
Component-Port => local signal

 

Testbench-Architecture

- The component under test is known
- Generate the Stimuli in a process
- Delay statement are **not** synthesizable. Dont worry!!! The testbench will never be synthesized !

```
...  
stimuli : PROCESS  
BEGIN
```

```
    tb_x1 <= '0';  
    tb_x2 <= '0';  
    WAIT FOR 10 ns;  
    tb_x1 <= '1';  
    WAIT FOR 10 ns;  
    tb_x1 <= '0' AFTER 5 ns;
```

```
....  
END PROCESS stimuli;
```

Signals and value assignment

Drive the signals for 10 ns

Set this values after 5 ns

Entry in Signal-Schedule List

Only tb_x1 contains
new values,
tb_x2 maintain
old values

Timing-Behavior

Timing can be modelled differently

- wait for
- after
- Sensitivity-list

Use of **Generic**-Parameters

Here: delayed assignment (Start-delay: *del_time: time*)

Parameter for time-delay with default value

```
ENTITY two_gate IS
  GENERIC( del_time: time := 2 ns );
  PORT( x1, x2: in std_logic; y: out std_logic );
END two_gate;
```

```
ARCHITECTURE two_gate_del_nand OF two_gate IS
  BEGIN
    y <= NOT ( x1 AND x2 ) AFTER del_time;
  END two_gate_del_nand ;
```

delayed assignment after 2ns

Simulation – vhdldbxb

vhdldbxb as Simulator (Synopsys)

- Selection of the entity under test
- **Hierarchy Browser**
- **Wave-Form-Viewer**

Alternative:

- **Modelsim** (Mentor Graphics- Free version for student)

Stimuli from the testbench (Test-Input)

Simulation result is the waveform of the reaction of component's signals to the stimuli.

The „Mean“ Vending Machine

```
entity G_Automat is
port (clk,reset, E, C,S7, R: in std_logic;
      GC, G7, M : out std_logic);
end G_Automat;

architecture Behavioral of G_Automat is
Type state_type is (I, H);
Signal current_state, next_state: state_type;
Begin
  comp:process (E, C, S7, R, current_state)
  begin
    case current_state is
      when I =>
        if (E = '1') then next_state <= H; else next_state <= I; end if;
      when H =>
        if (C= '1') then next_state <= I; M <= '0' ; GC <= '1' ; G7 <= '0';
        elsif (S7 = '1') then next_state <= I; M <= '0' ; G7 <= '1' ; G7 <= '0';
        elsif (R = '1') then next_state <= I; M <= '1' ; G7 <= '0'; G7 <= '0'; GC <= '0';
        elsif (E = '1') then next_state <= I; M <= '0' ; G7 <= '0'; GC <= '0' ;
        else next_state <= H; M <= '0' ; G7 <= '0'; GC <= '0'; end if;
    end case;
  ....
end;
```

The „Mean“ Vending Machine

Combinational Block

```
entity G_Automat is
port (clk,reset, E, C, S7, R: in std_logic;
      GC, G7, M : out std_logic);
end G_Automat;

architecture Behavioral of G_Automat is
Type state_type is (I, H);
Signal current_state, next_state: state_type;
Begin
  comp:process (E, C, S7, R, current_state)
  begin
    case current_state is
      when I =>
        if (E = '1') then next_state <= H; else next_state <= I; end if;
      when H =>
        if (C= '1') then next_state <= I; M <= '0' ; GC <= '1' ; G7 <= '0';
        elsif (S7 = '1') then next_state <= I; M <= '0' ; G7 <= '1' ; G7 <= '0';
        elsif (R = '1') then next_state <= I; M <= '1' ; G7 <= '0'; G7 <= '0'; GC <= '0';
        elsif (E = '1') then next_state <= I; M <= '0' ; G7 <= '0'; GC <= '0' ;
        else next_state <= H; M <= '0' ; G7 <= '0'; GC <= '0'; end if;
    end case;
  ....
end;
```

The „Mean“ Vending Machine

Register Block

....

```
reg: process(clk, next_state, reset)
begin
    if (reset = '1') then current_state <= I;
        elsif (clk'event and clk = '1') then
            current_state <= next_state;
        end if;
    end process;
end Behavioral;
```

The „Mean“ Vending Machine Testbench

```
ENTITY tb_g_automat IS
END tb_g_automat;

ARCHITECTURE testbench_arch OF tb_g_automat IS
    COMPONENT g_automat
        PORT (
            clk, reset, E, C, S7, R : In std_logic;
            GC, G7, M : Out std_logic
        );
    END COMPONENT;

    SIGNAL clk : std_logic := '0';
    SIGNAL reset : std_logic := '0';
    SIGNAL E : std_logic := '0';
    SIGNAL C : std_logic := '0';
    SIGNAL S7 : std_logic := '0';
    SIGNAL R : std_logic := '0';
    SIGNAL GC : std_logic := '0';
    SIGNAL G7 : std_logic := '0';
    SIGNAL M : std_logic := '0';

    BEGIN
        UUT : g_automat
            PORT MAP ( clk => clk, reset => reset, E => E,
                      C => C, S7 => S7, R => R, GC => GC,
                      G7 => G7, M => M );
    ...

    ...
    PROCESS      -- clock process for clk
    BEGIN
        CLOCK_LOOP : LOOP
            clk <= '0';
            WAIT FOR 20 ns;
            clk <= '1';
            WAIT FOR 20 ns;
        END LOOP CLOCK_LOOP;
    END PROCESS;

    PROCESS
    BEGIN
        reset <= '1';
        WAIT FOR 55 ns;
        reset <= '0';
        E <= '1';
        WAIT FOR 40 ns;
        E <= '0';
        R <= '1';
        WAIT FOR 40 ns;
        R <= '0';
        WAIT FOR 40 ns;
        E <= '1';
        WAIT FOR 40 ns;
        E <= '0';
        WAIT FOR 40 ns;
    END PROCESS;
```


The „Mean“ Vending Machine


...

```
S7 <= '1';  
  WAIT FOR 40 ns;  
  S7 <= '0';  
  WAIT FOR 40 ns;  
  E <= '1';  
  WAIT FOR 40 ns;  
  E <= '0';  
  WAIT FOR 40 ns;  
  E <= '1';  
  WAIT FOR 40 ns;  
  E <= '0';  
  WAIT FOR 40 ns;  
  E <= '1';  
  WAIT FOR 40 ns;  
  E <= '0';  
  WAIT FOR 40 ns;  
  C <= '1';  
  WAIT FOR 40 ns;  
  C <= '0';  
  WAIT FOR 40 ns;  
  C <= '1';  
  WAIT FOR 40 ns;  
  C <= '0';  
  WAIT FOR 345 ns;  
END PROCESS;  
END testbench_arch; ..
```



...

The „Mean“ Vending Machine

Signal Waveform

 

Want To Learn More ?

  

Consider Undergraduate
Research With Us/Other Labs

<https://smartsystems.ece.ufl.edu/>

